

Same we can verify that the op-amp is in negative feedback, so the Golden Rules gives:

$$i_+ = i_- = 0$$

$$V_+ = V_- = 0 \text{ (grounded } V_+)$$

Then, using KCL, so $i_R = i_+ + i_C \Rightarrow i_R = i_C$

Then, since $V_0 - V_+ = V_R = i_R \cdot R_1$ with $V_+ = 0$.

$$\text{so } i_C = i_R = \frac{V_0}{R_1}$$

$$\text{Now, } V_1 - V_+ = -V_{C1} \Rightarrow V_1 = -V_{C1} \quad (1)$$

which could be calculated by having $i_C = C_1 \frac{dV_{C1}}{dt} = \frac{V_0}{R_1}$

$$\Rightarrow \int_0^t dV_{C1} = \int_0^t \frac{V_0}{R_1 C_1} dt$$


$$\Rightarrow V_{C1}(t) - V_{C1}(0) = \frac{V_0}{R_1 C_1} (t - 0)$$

with $V_{C1}(0) = 0V$, so $V_{C1}(t) = \frac{V_0}{R_1 C_1} t$


$$\Rightarrow V_1 = -V_{C1} = \boxed{-\frac{V_0 \cdot t}{R_1 C_1}}$$

$$b) T_1 = T_2 = \frac{-V_{TH} - V_{TN}}{-\frac{V_{SAT}}{R_1 C_1}} = \frac{2V_{TH} R_1 C_1}{V_{SAT}}$$

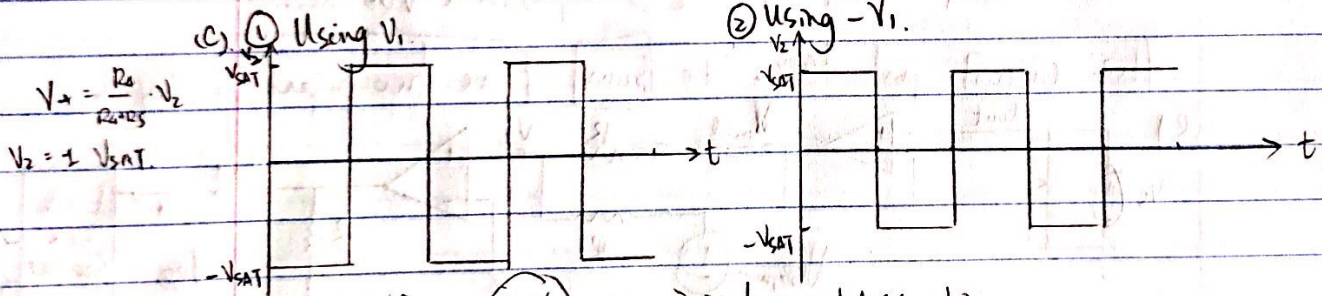by analyzing the eq 1 line and its slope given.



With $-V_1$ as input matches (b)

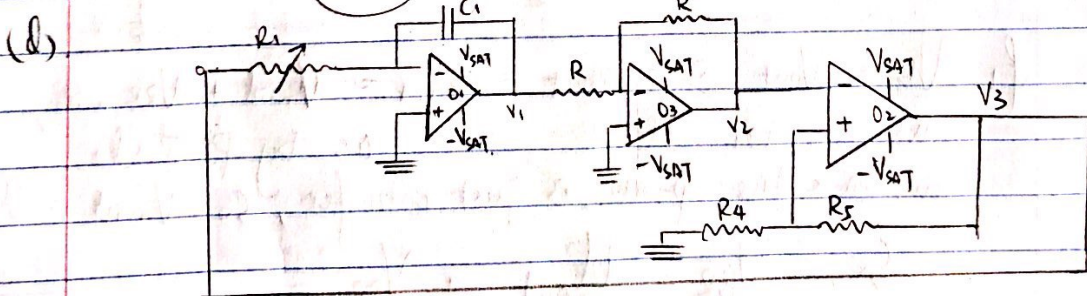

(e) First, $+V_{TH} = \frac{R_4}{R_4 + R_5} V_{SAT}$. with $+V_{SAT} = 10V$, $C_1 = 0.01mF$, $R_4 = 10k\Omega$, and $+V_{TH} = 5V$, so $R_5 = 10k\Omega$.

Then, since we wish to have $f = 1kHz$, so $t = \frac{1}{f} = 1ms$.


So $R_1 C_1 = 1ms$, with $C_1 = 0.01mF$,

so $R_1 = 100\Omega$

$$\Rightarrow \boxed{R_1 = 100\Omega, R_5 = 10k\Omega}$$

2. (a) $\bigcirc I_s$ $\bigcirc V_s$ $\bullet R_1$ $\bigcirc R_2$ $\bigcirc R_3$ $\bigcirc R_4$
 (MT Q3) (b) $\bullet U_1$ $\bullet U_2$ $\bullet U_3$ $\bigcirc U_4$ $\bigcirc U_5$ $\bigcirc U_6$
 (c) $U_5 - U_4 = i_3 R_3$
 (d) $i_3 + i_2 - i_4 = 0$

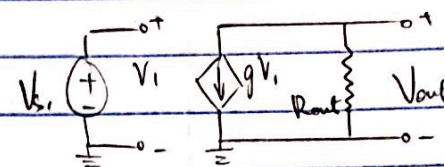3. (a) Due to the direction of the current,
 (MT Q4) we have that $V_{out,1} = -gV_1 R_{out}$.
 Then, $V_1 = V_{s1}$, so $V_{out,1} = -gV_{s1} R_{out}$



(b) Similarly, $V_{out,2} = -gV_2 R_{out} = -gV_{s2} R_{out}$

(c) Thus, $V_{out} = V_{out,1} + V_{out,2} = -gV_{s1} R_{out} - gV_{s2} R_{out}$

With $g = \frac{1}{R_{out}}$, so $V_{out} = -V_{s1} - V_{s2}$

(d) Now, $V_{Th} = V_{out} = -V_{s1} - V_{s2}$ as calculated in part (c).


Then, we can zero all the independent sources and calculate I_{test}

So $V_1 = V_2 = V_{s1} = V_{s2} = 0V$, so $gV_1 = gV_2 = 0(A)$.

Supplying a V_{test} , we have $I_{test} = \frac{V_{test}}{R_{out}}$

So $R_{Th} = \frac{V_{test}}{I_{test}} = R_{out}$

Thus, the Thevenin equivalent is:

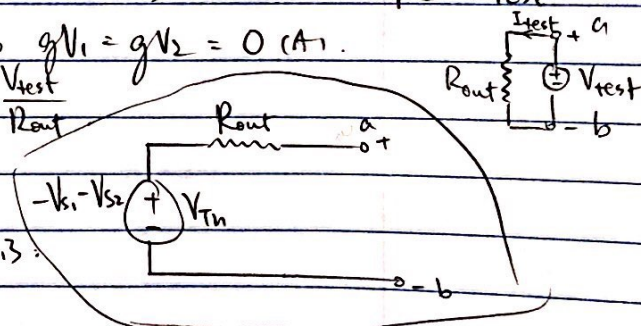

4. (a) Using voltage divider, $V_{Daisy} = \frac{4k\Omega}{4k\Omega + 4k\Omega} \cdot 1kV = 500V$.

(MT Q5).

So $W_{Daisy} = \frac{V_{Daisy}^2}{R_{Daisy}} = \frac{(500V)^2}{4k\Omega} = 62.5W > 10W = W_{breakdown}$.

So, Daisy is not safe.



(b) $R_{eq} = R_{free} \parallel R_{Daisy} \parallel R_{Bilton} = 4k\Omega \parallel 4k\Omega \parallel 2k\Omega = 1k\Omega$
 $\Rightarrow V_{Daisy} = V_{Bilton} = \frac{1k\Omega}{4k\Omega + 1k\Omega} \cdot 1kV = 200V$ using voltage divider.

$\Rightarrow W_{Daisy} = \frac{V_{Daisy}^2}{R_{Daisy}} = \frac{(200V)^2}{4k\Omega} = 10W \leq W_{Daisy, breakdown}$

$W_{Bilton} = \frac{V_{Bilton}^2}{R_{Bilton}} = \frac{(200V)^2}{2k\Omega} = 20W \leq 25W = W_{Bilton, breakdown}$

Thus, Both Daisy and Bilton are safe.

5. (12T Q6)

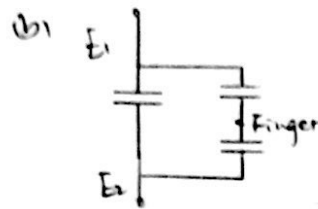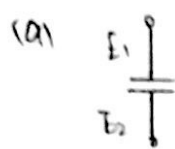

(c) $C = \epsilon \frac{A}{d}$
 $= (12 \text{ fF/mm} + n \text{ fF/mm}) \cdot \frac{A}{d}$
 $= \left[(12+n) \cdot \frac{A}{d} \text{ fF/mm} \right]$

(1) i. This is when the finger is touching,

So $C_{\text{touch}} = C_{\text{no touch}} + (C_{F-E1} \parallel (C_{F-E1L} + C_{F-E2R}))$
 $= (12+n) \cdot \frac{4 \text{ mm}^2}{2 \text{ mm}} \text{ fF/mm} + 8 \text{ fF} \parallel (4 \text{ fF} + 4 \text{ fF})$
 $= (24 + 2n) \text{ fF} + 4 \text{ fF} = \boxed{(28 + 2n) \text{ fF}}$

(2) No touch is when the other branch is open circuit,

So $C_{\text{no touch, eq}} = C_{\text{no touch}} = \boxed{(24 + 2n) \text{ fF}}$

Thus, we can calculate. $\frac{(28+2n) \text{ fF} - (24+2n) \text{ fF}}{(24+2n) \text{ fF}} \geq 10\%$
 for the display to work:

$\Rightarrow 4 \geq 2.4 + 0.2n$

So $n \leq 8$

Thus, maximum fire times is $\boxed{8}$

6(a), Since $I_c = -I_{PD}$ and $I_c = C_{PD} \cdot \frac{dV_{PD}}{dt}$
 (12T Q7)


So $-I_{PD} = C_{PD} \cdot \frac{dV_{PD}}{dt}$


$\Rightarrow \int_0^t \frac{-I_{PD}}{C_{PD}} dt = \int_0^t dV_{PD}$

$\Rightarrow -\frac{I_{PD}}{C_{PD}} (t-t_0) = V_{PD}(t) - V_{PD}(0)$

and given that $V_{PD}(t_{z0}) = V_{DD}$,

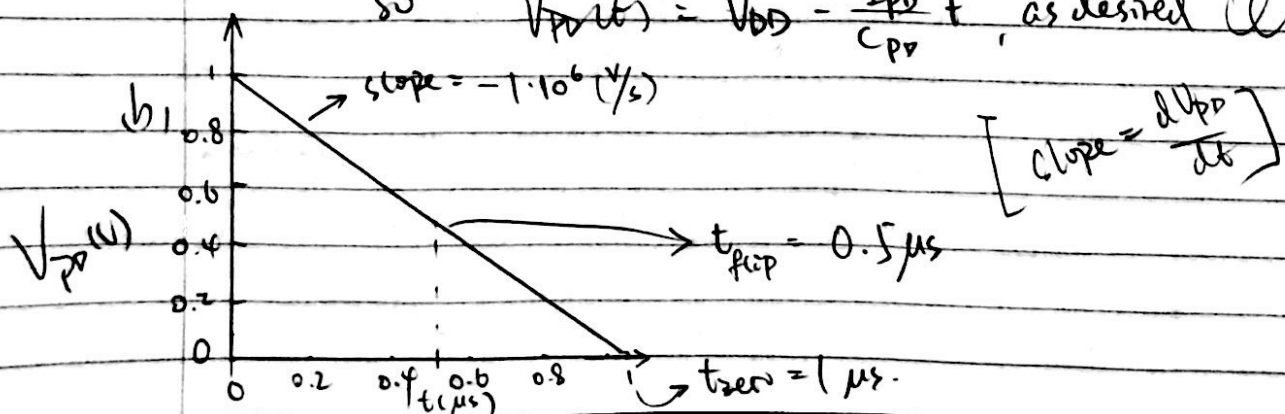So $V_{PD}(t) = V_{DD} - \frac{I_{PD}}{C_{PD}} t$, as desired (Q.E.D.)



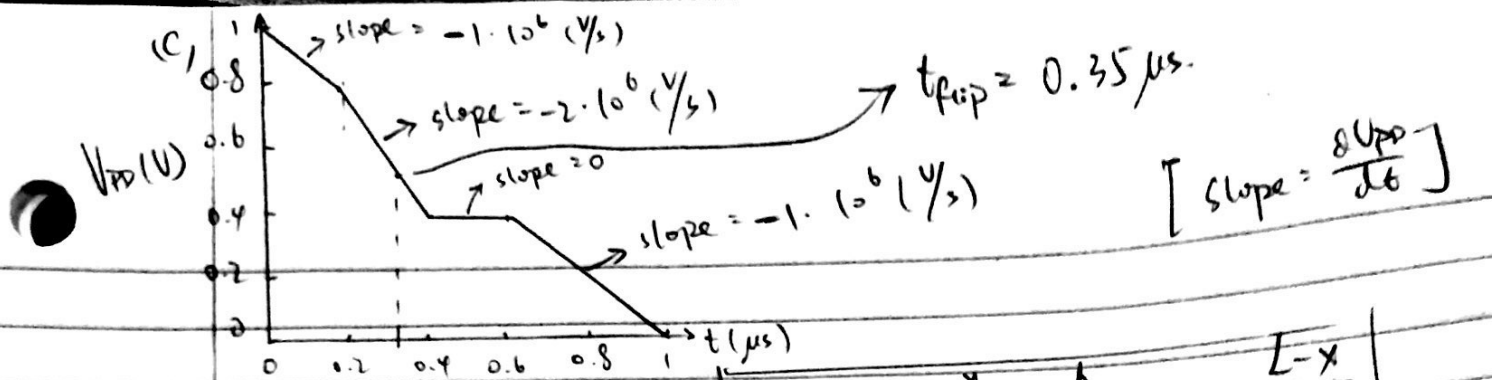


7. (MT a8) (a) Since $R = \rho \frac{L}{A}$, so $R_{\text{bottom}} = \rho \frac{x}{A}$, $R_{\text{top}} = \rho \frac{L-x}{A}$

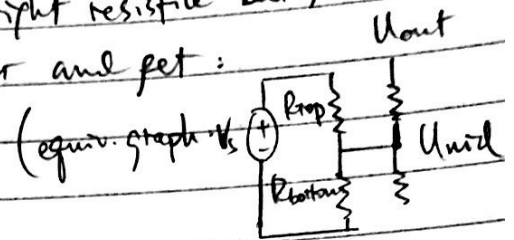(b) Since there's no current through the right resistive bar,

so we can use just a voltage divider and get:

$$U_{\text{mid}} = U_{\text{out}} = \frac{R_{\text{bottom}}}{R_{\text{top}} + R_{\text{bottom}}} V_s$$



(c) No because U_{out} can go as low as 0V with $x \rightarrow 0$. But $V_{BB, \text{min}} > 0$, so we can't utilize the full range.


(d) First $V_+ = \frac{R}{2+R} V_{\text{in}} + \frac{R}{2+R} V_{BB, \text{min}}$

$$= \frac{1}{2} (V_{\text{in}} + V_{BB, \text{min}})$$

Then, using formula for a non-inverting negative feedback op-amp,

$$\text{so } V_{\text{out}} = V_+ \cdot \left(1 + \frac{R}{R}\right) = V_{\text{in}} + V_{BB, \text{min}}$$

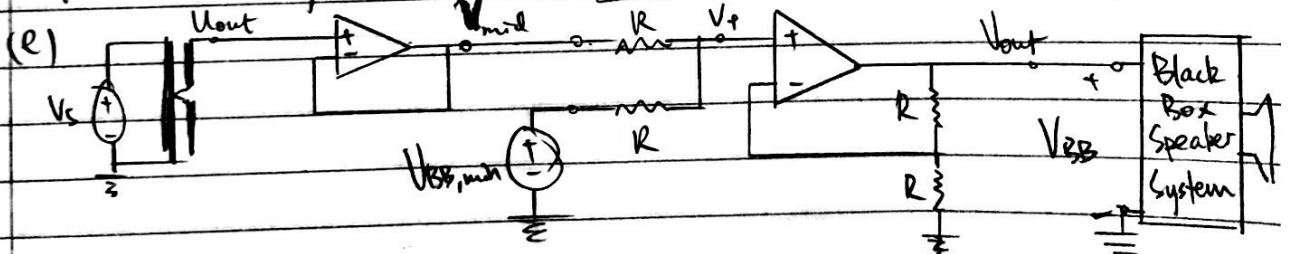This circuit just takes the Sum of the two input voltages.



f) $V_{BB} = V_{\text{out}} - 0 = V_{\text{out}} = 2V_+ = U_{\text{mid}} + V_{BB, \text{min}}$
 as by part (d).

Then, since the op-amp is just a buffer, so $U_{\text{mid}} = U_{\text{out}}$.

$$\text{So, } V_{BB} = U_{\text{out}} + V_{BB, \text{min}}$$

$$= \frac{R_{\text{bottom}}}{R_{\text{top}} + R_{\text{bottom}}} V_s + V_{BB, \text{min}} = \left[\frac{x}{L} V_s + V_{BB, \text{min}} \right]$$

g) I'd like "like"

⇒ 8. I worked alone without help, except memory from MT and Discussion.

1. (a). Write KCL at V^- assuming all currents are leaving,

$$\text{So } i_{R_1} = -i_{C_1}$$

$$\text{So } i_{C_1} = C_1 \frac{d(0 - V_1(t))}{dt}$$

$$\text{So, } -\frac{V_0 - 0}{R_1} = C_1 \frac{dV_1(t)}{dt} \Leftrightarrow \int -\frac{V_0}{R_1 C_1} dt = \int dV_1(t)$$

$$\text{Thus, } V_1(t) = \boxed{-\frac{1}{R_1 C_1} \int_0^t V_0 d\tau}$$

(e). $V_{TH} = \frac{R_4}{R_4 + R_5} V_{SAT}$, since $\pm V_{TH} = \pm 5V$, $V_{SAT} = 10V$, $R_4 = 10k\Omega$

$$\text{So } \boxed{R_5 = 10k\Omega}$$

Now, $T_1 = R_1 C_1 \frac{2V_{TH}}{V_{SAT}}$ and $T_1 + T_2 = \frac{1}{1kHz} = 1ms$, $T_1 = T_2$
 $\Rightarrow T_1 = 0.5ms$

$$\text{So } 0.5ms = R_1 \cdot 0.01mF \cdot \frac{2 \cdot 5V}{10V} \Rightarrow \boxed{R_1 = 50\Omega}$$