


5. Multitouch Resistive Touchscreen

(a) $4k\Omega$

Since $W = 3cm = 0.03m$, $H = 12cm = 0.12m$, $T = 1mm = 1 \cdot 10^{-3}m = 0.001m$, so we can calculate the resistance between E_1 and E_2 as:

$$R = \rho \cdot \frac{L}{A} = \rho \cdot \frac{H}{W \cdot T} = 1\Omega m \cdot \frac{0.12m}{0.03m \cdot 0.001m} = 4000\Omega = 4 \text{ k}\Omega$$

1b)

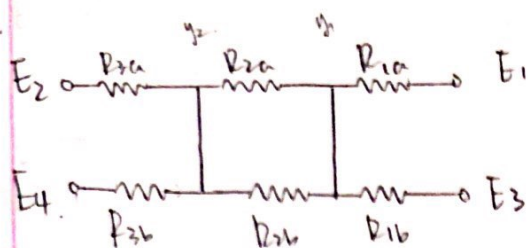


Given that $R_{total} = l \frac{H}{W \cdot T} = 8 \text{ k}\Omega$, $y_1 = 3 \text{ cm}$, $y_2 = 7 \text{ cm}$, $H = 12 \text{ cm}$
 with $R_{total} = 8 \text{ k}\Omega$,
 so $R_{1a} = R_{1b} = R_{total} \cdot \frac{y_1}{H} = 2 \text{ k}\Omega$

$$R_{2a} = R_{2b} = R_{total} \cdot \frac{y_2 - y_1}{H} = 2.667 \text{ k}\Omega$$

$$R_{3a} = R_{3b} = R_{total} \cdot \frac{H - y_2}{H} = 3.333 \text{ k}\Omega$$

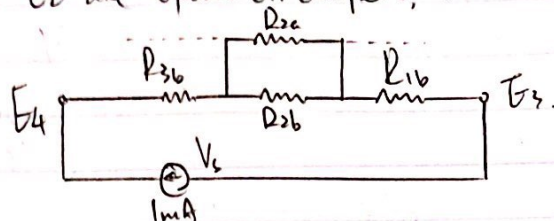(c) Using the given conditions, since E_1 and E_2 are open-circuited, so no current flow through resistors R_{2a} and R_{1a} , which means that the circuit diagram is equivalent to:



We can calculate using methods that the resistance between E_4 and E_3 is:

$$R_{eq} = R_{3b} + \frac{1}{\frac{1}{R_{2a}} + \frac{1}{R_{2b}}} + R_{1b} = R_{total} \cdot \frac{H - y_2}{H} + \frac{1}{2} \cdot R_{total} \cdot \frac{y_2 - y_1}{H} + R_{total} \cdot \frac{y_1}{H}$$

with $y_1 = 3 \text{ cm}$, $y_2 = 7 \text{ cm}$, $H = 12 \text{ cm}$, so $= R_{total} \cdot \frac{H - y_2/2 + y_1/2}{H} = \frac{20}{3} \text{ k}\Omega = 6.667 \text{ k}\Omega$

Thus, $V_s = I_s \cdot R_{eq} = 1 \text{ mA} \cdot 6.667 \text{ k}\Omega = 6.667 \text{ V}$.

which means that $V_{E_4 - E_3} = V_s = \boxed{6.667 \text{ V}}$

(d) Using what we've deduced in the steps of part (c), we have that:

$$R_{eq} = R_{total} \cdot \frac{H - y_2/2 + y_1/2}{H}$$

So, $V_{E_4 - E_3} = V_s = I_s \cdot R_{eq} = 1 \text{ mA} \cdot 8 \text{ k}\Omega \cdot \frac{H - y_2/2 + y_1/2}{H} = 8 \text{ V} \cdot \left(1 - \frac{y_2}{24} + \frac{y_1}{24}\right)$

So, $\boxed{V_{E_4 - E_3} = \left(8 - \frac{1}{3}y_2 + \frac{1}{3}y_1\right) \text{ V}}$

(e) Using similar logic from part (c) and (d), so we can drive E_2, E_4 with a 1 mA current source and measure $V_{E_4 - E_2} = I_s \cdot R_{eq_{2,4}}$ where

$$R_{eq_{2,4}} = R_{3a} + \frac{1}{\frac{1}{R_{2a}} + \frac{1}{R_{3b}}} + R_{2b} = R_{total} \cdot \left(\frac{H - y_2}{H} + \frac{1}{2} \cdot \frac{y_2 - y_1}{H} + \frac{H - y_2}{H}\right)$$

$$= 8 \text{ k}\Omega \cdot \frac{2H - \frac{3}{2}y_2 - \frac{1}{2}y_1}{H}$$

So, $V_{E_4 - E_2} = 1 \text{ mA} \cdot 8 \text{ k}\Omega \cdot \left(2 - \frac{3}{24}y_2 - \frac{1}{24}y_1\right) = \left(16 - y_2 - \frac{1}{3}y_1\right) \text{ V}$

Similarly, $R_{eq1,3} = R_{1a} + \frac{1}{\frac{1}{R_{2a}} + \frac{1}{R_{2b}}} + R_{1b} = R_{total} \cdot \left(\frac{y_1}{H} + \frac{1}{2} \cdot \frac{y_2 - y_1}{H} + \frac{y_1}{H} \right)$

$$= 8k\Omega \cdot \left(\frac{y_1 + \frac{1}{2}y_2 - \frac{1}{2}y_1 + y_1}{H} \right) \text{ where } H = 12 \text{ (cm)}$$

$$= 8k\Omega \cdot \left(\frac{1}{8}y_1 + \frac{1}{24}y_2 \right)$$

And, providing/driving E_1, E_3 with a 1mA current source gives:

$$V_{E_1 - E_3} = I_s R_{eq1,3} = 1mA \cdot 8k\Omega \left(\frac{1}{8}y_1 + \frac{1}{24}y_2 \right)$$

$$\text{So } V_{E_1 - E_3} = \left(y_1 + \frac{1}{3}y_2 \right) V$$

Thus, we have two (plus one) equations:

$$V_{E_4 - E_2} = \left(16 - \frac{1}{3}y_1 - y_2 \right) V$$

$$V_{E_1 - E_3} = \left(y_1 + \frac{1}{3}y_2 \right) V$$

$$[\text{from (1)}] \quad V_{E_4 - E_3} = \left(8 + \frac{1}{3}y_1 - \frac{1}{3}y_2 \right) V$$