

EECS 16A      Designing Information Devices and Systems I      Midterm 2  
Spring 2018

Exam Location: 100 Genetics & Plant Bio Last Name: Lazich - Melville

PRINT your student ID: \_\_\_\_\_

PRINT AND SIGN your name: \_\_\_\_\_, \_\_\_\_\_ \_\_\_\_\_  
(last name) (first name) (signature)

PRINT your discussion section and GSI(s) (the one you attend): \_\_\_\_\_

Name and SID of the person to your left: \_\_\_\_\_

Name and SID of the person to your right: \_\_\_\_\_

Name and SID of the person in front of you: \_\_\_\_\_

Name and SID of the person behind you: \_\_\_\_\_

**1. What do you enjoy most about EE16A? (1 Point)**


**2. What other courses are you taking this semester? (1 Point)**

Do not turn this page until the proctor tells you to do so. You may work on the questions above.

PRINT your student ID: \_\_\_\_\_

### 3. Seven Steps of Highly Resistive Circuits (10 points)

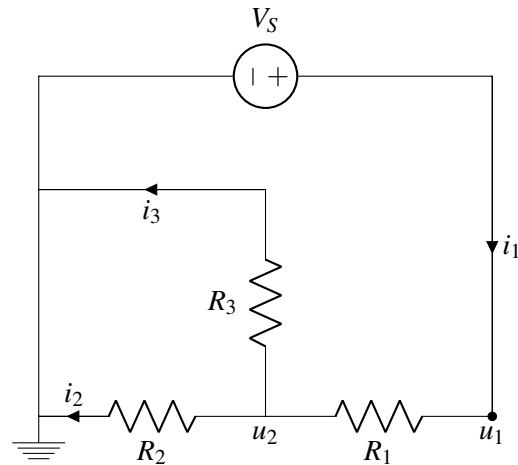- (a) (3 point) Label the +/- polarity of voltage across each resistor element on the following circuit. Be sure to follow passive sign convention using the labeled currents.



- (b) (7 points) Fill in the following matrix and unknown vector, such that they represent linearly independent equations for the circuit given above. Assume the resistor and voltage source values are known constants. **You do not need to solve this matrix.**

$$\begin{bmatrix} \phantom{0} \\ \phantom{0} \\ \phantom{0} \\ \phantom{0} \\ \phantom{0} \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \\ u_1 \\ u_2 \end{bmatrix} = \begin{bmatrix} \phantom{0} \\ \phantom{0} \\ \phantom{0} \\ \phantom{0} \\ \phantom{0} \end{bmatrix}$$

PRINT your student ID: \_\_\_\_\_


#### 4. "Operational" Amplifiers (12 points)

“As an amplifier so connected can perform the mathematical operations of arithmetic and calculus on the voltages applied to its inputs, it is hereafter termed an ‘operational amplifier’.”

John Ragazzini, Robert Randall and Frederick Russell  
Proceedings of IRE, Vol. 35, May 1947

In this problem we will explore some of the mathematical operations an op amp can perform.

(a) (5 points)

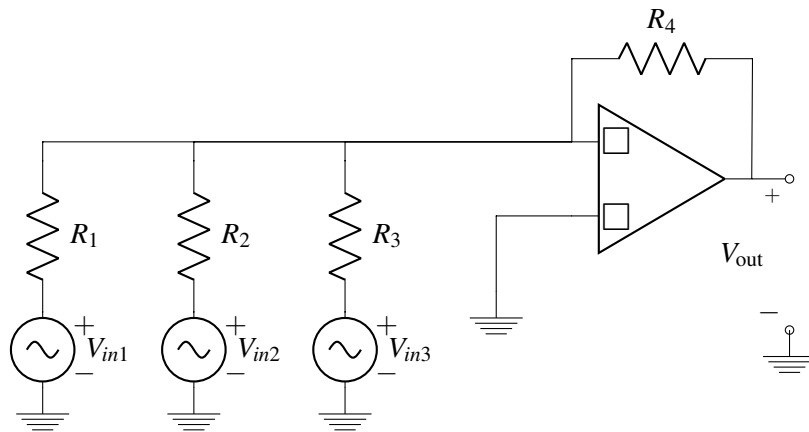


- Label the ‘+’ and ‘−’ terminals of the op amp above so that it is in negative feedback.
- Derive an expression for  $V_{out}$  as a function of  $V_{in1}$ ,  $V_{in2}$ , and  $V_{in3}$ .

- Mark the operation below that is best represented by this configuration.

☐ Subtraction
 ☐ Inner Product
 ☐ Differentiation
 ☐ Integration

(b) (7 points)

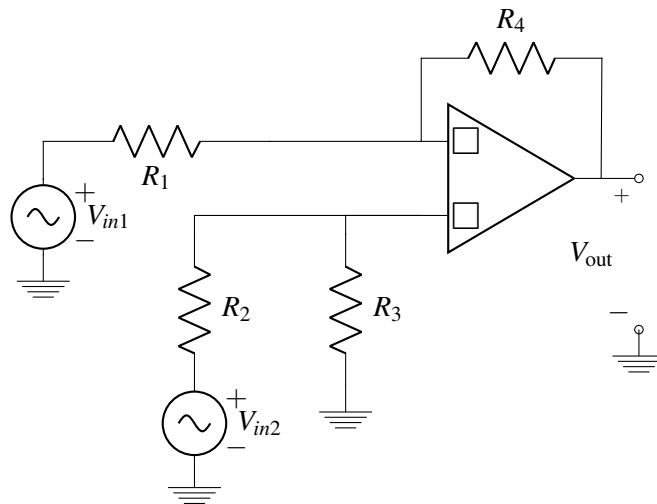


- Label the '+' and '-' terminals of the op amp above so that it is in negative feedback.
- Derive an expression for  $V_{out}$  as a function of  $V_{in1}$  and  $V_{in2}$ .

PRINT your student ID: \_\_\_\_\_

**5. Equivalent Capacitance (9 points)**

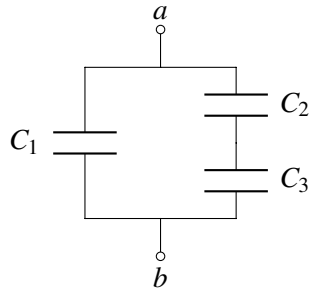- (a) (4 points) Find the equivalent capacitance between terminals  $a$  and  $b$  of the following circuit in terms of the given capacitors  $C_1$ ,  $C_2$ , and  $C_3$ . Leave your answer in terms of the addition, subtraction, multiplication, and division operators **only**.




- (b) (5 points) Find and draw a capacitive circuit using three capacitors,  $C_1$ ,  $C_2$ , and  $C_3$ , that has equivalent capacitance of

$$\frac{C_1(C_2 + C_3)}{C_1 + C_2 + C_3}$$

PRINT your student ID: \_\_\_\_\_

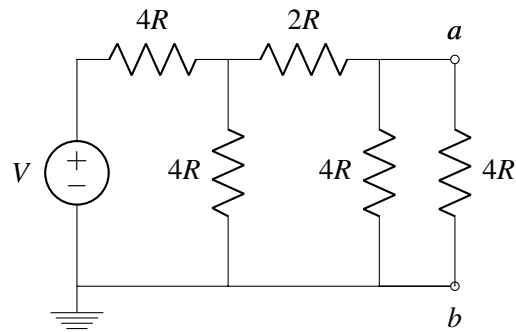**6. Power to Resist (6 points)**


Find the power dissipated by the voltage source in the circuit below. Be sure to use passive sign convention.




PRINT your student ID: \_\_\_\_\_

**7. Mechanical Thevenin and Norton Equivalents (10 points)**

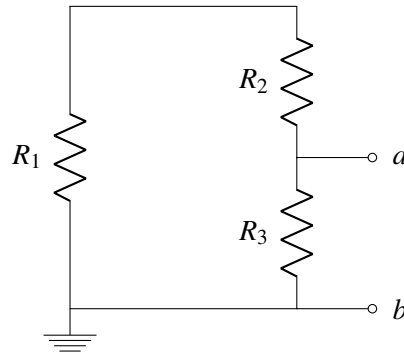- (a) (4 points) Find and draw the **Thevenin** equivalent circuit between terminals  $a$  and  $b$  in the circuit below. Clearly label the Thevenin equivalent voltage,  $V_{th}$ , and the Thevenin equivalent resistance  $R_{th}$ .



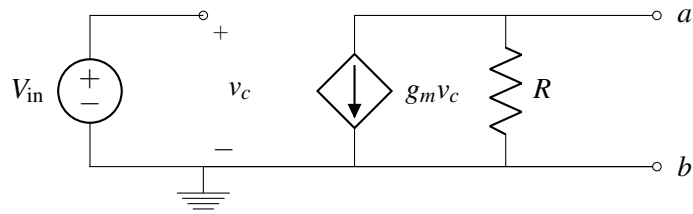- (b) (6 points) Find and draw the **Norton** equivalent circuit between terminals  $a$  and  $b$  in the circuit below. Clearly label the Norton equivalent current,  $I_{no}$ , and the Norton equivalent resistance  $R_{no}$ .






PRINT your student ID: \_\_\_\_\_

### 8. Midterms are a lot of Pressure (16 points)

In our labs, we used our resistive touchscreen to figure out where we were pressing in a 2D space. Now we'll use a new setup to determine how hard we're pressing! For this we'll use something called "pressure sensitive rubber," which incorporates conductive rubber and metal into one system. As the rubber is pressed, the conductive rubber portions are compressed, which changes the resistance. The metal plates do not change, but they assist in conduction through the material.

The pressure sensitive rubber system is shown below, with a resistive model next to the diagram. The resistivity of rubber and metal are represented by  $\rho_R$  and  $\rho_M$  respectively. When the system is at rest (no touch), the resistances of the rubber and metal are represented by  $R_R$  and  $R_M$ . The area of the sensor, as seen from above, is  $A$ .

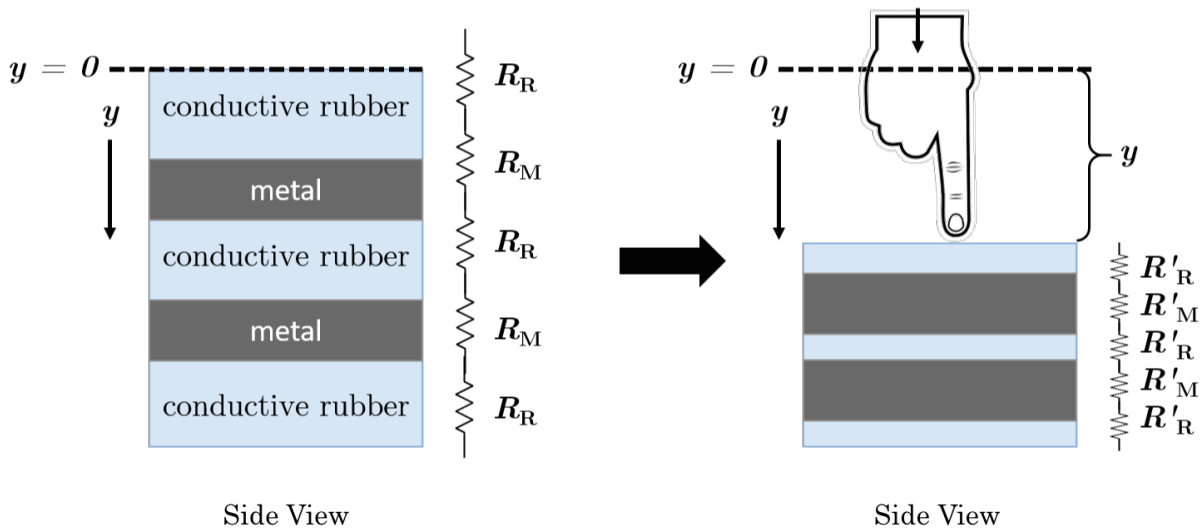To use the material, a finger presses on top of the system, compressing the rubber regions, creating a change in resistance, also shown below. Please answer the following questions related to the system.



- (a) (2 point) Is the resistor model implementing resistors in series or parallel?

- (b) (3 points) If the values are  $R_R = 1 \text{ k}\Omega$  and  $R_M = 10 \Omega$ , what is the total resistance before pressing the system?

- (c) (4 points) During the press, the length of each rubber portion is reduced by a factor of 5. (Its length is now 1/5 of its original value.) The size of the metal plates does not change. What is the new total resistance during a press?

- (d) (5 points) The force required to compress the rubber is  $F = ky$ , where  $k$  is a constant and  $y$  is the distance compressed (from the origin). Derive an expression for the resistance as a function of the pressing force  $F$ . Write your answer in terms of the initial resistances ( $R_R$  and  $R_M$ ), the resistivities ( $\rho_R$  and  $\rho_M$ ), the area of the sensor,  $A$ , and the constant,  $k$ . Assume all rubber layers compress the same amount and uniformly.

- (e) (2 points) For a particular sensor, we find that the resistance is:

$$R(F) = \frac{8k\Omega \cdot \text{mm}^2}{A} - \left(100 \frac{\Omega \cdot \text{m}^2}{\text{N}}\right) \frac{F}{A}$$

We define the sensitivity of the sensor,  $S$ , to be the change in resistance per unit of force:


$$S = \left| \frac{dR}{dF} \right|$$

If we want to increase sensitivity, how should we change the area of the sensor? Justify your answer in 1-2 sentences.

PRINT your student ID: \_\_\_\_\_
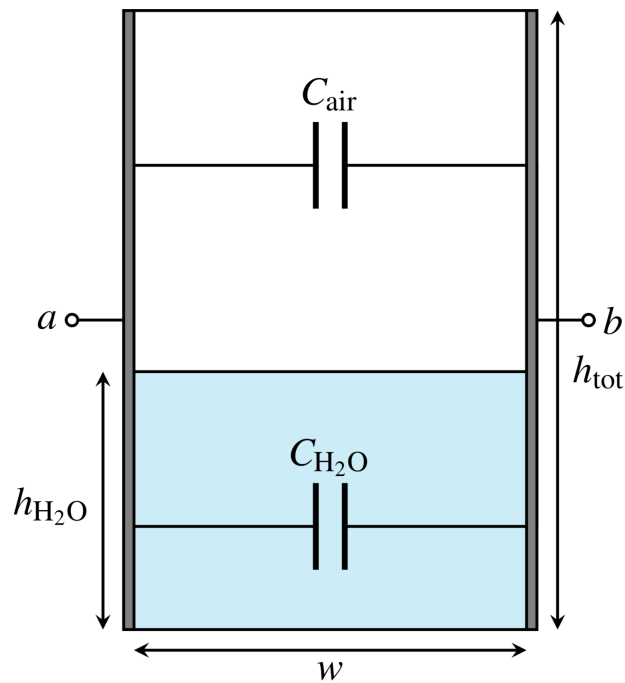
### 9. Rain Sensor (20 points)


A capacitive sensor can be used to measure how much rain water is in a tank. To do this, two capacitor plates are attached to a rectangular tank. The idea is to make a capacitor whose capacitance varies with the amount of water inside. The width and length of the tank are both  $w$  (i.e. the base is square), and the height of the tank is  $h_{\text{tot}}$ . The permittivity of air is  $\epsilon$ , and the permittivity of rainwater is  $81\epsilon$ .



- (a) (5 points) Derive an expression for the total capacitance,  $C_{\text{tank}}$ , between terminals  $a$  and  $b$  as a function of  $h_{\text{tot}}$ ,  $w$ ,  $h_{\text{H}_2\text{O}}$ , and  $\epsilon$ .

**Only this part is in scope for Q9**

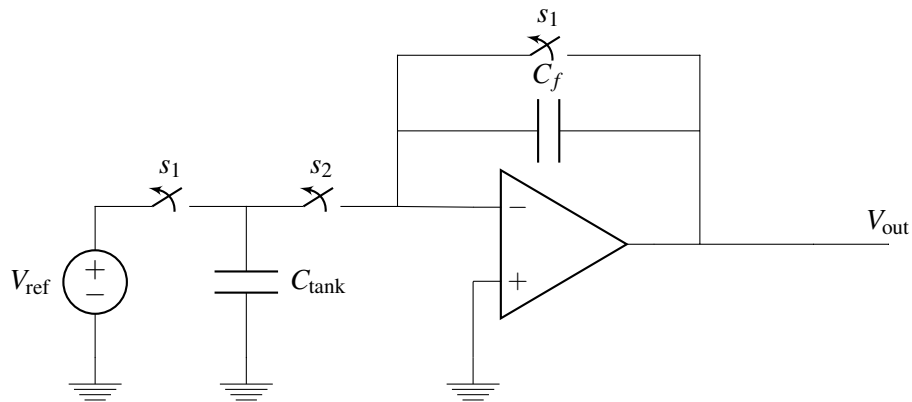- (b) (2 points) You would like to measure changes in  $C_{\text{tank}}$  as changes in voltage, so you design the following circuit. Draw the equivalent circuit when  $s_1$  is on and  $s_2$  is off.



- (c) (3 points) Find expressions for charge across each capacitor when  $s_1$  is on and  $s_2$  is off.

(d) (2 points) Draw the equivalent circuit when  $s_2$  is on and  $s_1$  is off.

(e) (3 points) Find expressions for charge across each capacitor when  $s_2$  is on and  $s_1$  is off.


(f) (5 points) Express  $V_{out}$  as a function of  $V_{ref}$  and the capacitances. What happens to  $V_{out}$  when the amount of water in the tank increases?

PRINT your student ID: \_\_\_\_\_

**10. A Light Design Problem, So to Speak... (15 points)**

Your pet cactus needs a lot of light every day, and you're not sure your room is sunny enough. You decide to use your knowledge from 16A to build a device to detect if the sun is shining in your room.

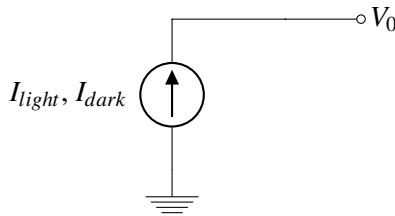- (a) (8 points) Assume you just finished the Imaging Lab, where you build a light sensor, which can be modeled as a current source as shown below. When the light is on, the current source produces 5 mA. When the light is off, 1 mA.



$$I_{light} = 5 \text{ mA}, I_{dark} = 1 \text{ mA}$$

Using this knowledge, **design a circuit that outputs 10 V when the light is on and 0 V when the light is off**. In addition to the model of the light sensor above, you may use the following components (only!):

- **one** op amp
- **one** resistor
- **two** voltage sources

You must explicitly note the power supplies used on the op amp. Clearly label values of resistors and voltage sources that you use.

- (b) (4 points) You realize that the light sensor can only provide a maximum of  $P_{max} = 40mW$  of power. Does this affect your design from part (a)? If so, how should it change? If not, why does it not affect it?  
(Do not use additional components beyond those specified in the problem statement.)

- (c) (3 points) You notice that there is noise in both  $I_{light}$  and  $I_{dark}$  (ie. sometimes the currents are higher or lower than expected). Assuming that there is the same amount of noise in both  $I_{light}$  and  $I_{dark}$ , modify your design to be as robust as possible to these fluctuations. Justify your design choices in 1-2 sentences. If you believe your design does not need modification, explain why.  
(Do not use additional components beyond those specified in the problem statement.)

PRINT your student ID: \_\_\_\_\_

Extra page for scratchwork.  
**Work on this page will NOT be graded.**



PRINT your student ID: \_\_\_\_\_

Doodle page!

Draw us something if you want or give us suggestions, compliments, or complaints.  
You can also use this page to report anything suspicious that you might have noticed.