

Exam location: RSF Back Left, last SID# 1, 4, + 5

PRINT your student ID: _____

PRINT AND SIGN your name: _____, _____
(last) (first) (signature)

PRINT your Unix account login: ee16a-_____

PRINT your discussion section and GSI (the one you attend): _____

PRINT your lab GSI (the one you attend): _____

Row Number (front row is 1): _____ Seat Number (left most is 1): _____

Name and SID of the person to your left: _____

Name and SID of the person to your right: _____

Name and SID of the person in front of you: _____

Name and SID of the person behind you: _____

Section 0: Pre-exam questions (3 points)

- 1. What are you looking forward to the most this summer? (1 pt)**
- 2. What was your favorite lab/homework problem/discussion WS in 16A? What did you like the most about it? (2 pts)**

Do not turn this page until the proctor tells you to do so. You can work on Section 0 above before time starts.

Section 1: Context-free questions


Unless told otherwise, you must show work to get credit. There will be very little partial credit given in this section.

3. Determinants (5 pts)

Compute the determinant of $\mathbf{A} = \begin{bmatrix} 2 & 6 & 2 \\ 1 & 2 & 1 \\ 2 & 6 & 4 \end{bmatrix}$.


4. Revenge of the Boxes (10 pts)

Consider the following circuit:

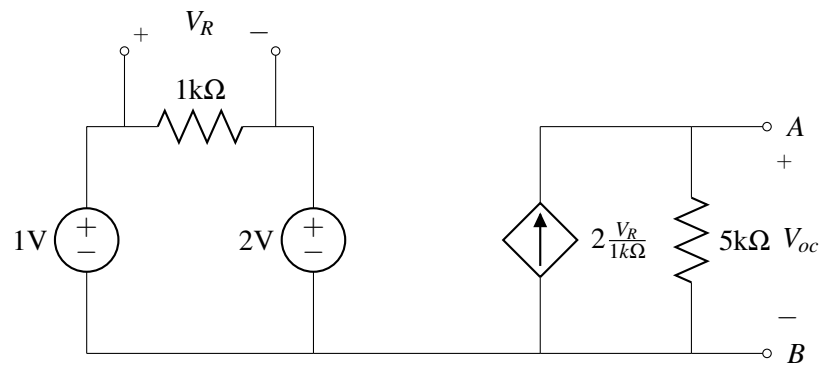

- (a) Find the open-circuit voltage V_{oc} between nodes A and B.
- (b) Find the short-circuit current I_{sc} between the same two points.

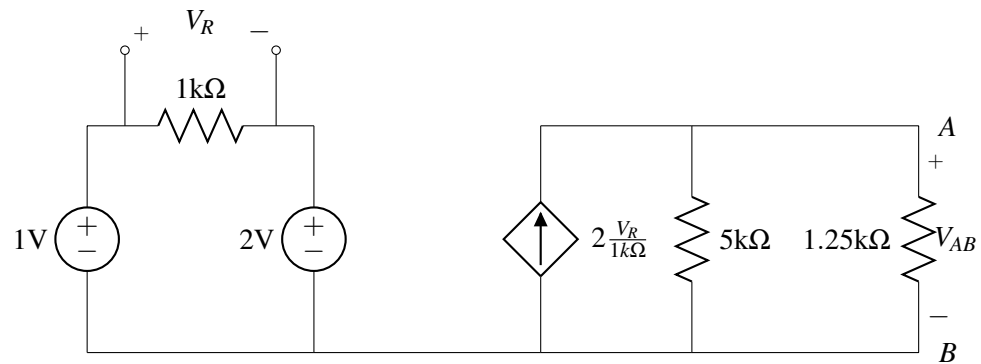- (c) Now assume that V_{oc} and I_{sc} are as written in the boxes below. (Note that these may or may not be the correct answer to the previous parts.) If you attach a $1.25\text{ k}\Omega$ resistor across nodes A and B (as shown below), what will be the value of the voltage V_{AB} (also defined below)?



V_{oc}	$-10V$
I_{sc}	$-2mA$

5. Full Bases (5 pts)

Let the orthonormal vectors $\vec{v}_1, \vec{v}_2, \vec{v}_3$ be a basis \mathcal{B} . Provide a simple (symbolic) expression for the vector \vec{x} (given below) as coordinates in the basis \mathcal{B} .

$$\vec{x} = \begin{bmatrix} 1 \\ 3 \\ -2 \end{bmatrix}$$

6. Bulletproof (10 pts)

- (a) Let \mathbf{A} and \mathbf{B} be diagonalizable $n \times n$ matrices. Show that if \mathbf{A} and \mathbf{B} have the same set of eigenvectors, then $\mathbf{AB} = \mathbf{BA}$.

- (b) Consider a symmetric $n \times n$ matrix \mathbf{A} . Show that if $\vec{x}^\top \mathbf{A} \vec{x} > 0$ for all $\vec{x} \neq \vec{0}$, then all eigenvalues of \mathbf{A} are positive. Fill in the blanks to complete the proof:

Let \vec{x} be a/an _____ of \mathbf{A} .

$$\mathbf{A}\vec{x} = \underline{\hspace{2cm}}$$

$$\vec{x}^\top \mathbf{A} \vec{x} = \underline{\hspace{2cm}} = \underline{\hspace{2cm}} (1)$$

We can rewrite _____ (1) with a summation: _____ (2).

Expression (2) is equivalent to $\vec{x}^\top \mathbf{A} \vec{x}$, and thus must be strictly positive. Explain in a single sentence why this means that any eigenvalue of \mathbf{A} must be positive.

Section 2: Free-form Problems


7. EEcology (22 pts)

In this problem we will study the evolution of a hypothetical ecosystem. Within an ecosystem, one can have all sorts of classifications of life forms. For example, your model could initially include only Herbivores and Plants. We will use what's called a "replacement model" to represent the dynamics of the ecosystem. Specifically, at every time step, some fraction of Plants is "eaten" by Herbivores, and the number of Herbivores increases by the number of Plants that were eaten. In addition, some fraction of Herbivores die, and, in the context of this problem, they become Plants. Finally, for both types of organisms, some fraction of the organisms remain in their current state. These same rules apply to new organisms introduced in the problem later on.

Note that throughout this problem, the total number of organisms remains the same. In other words, no organism can leave or enter the system.

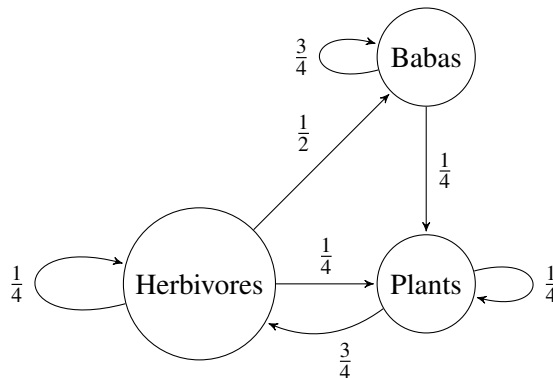
- (a) A new species of killer snake, the Baba Konstrictor, slithers its way into this peaceful environment. Babas are incredibly intelligent and hunt Herbivores. The new ecology network is depicted below.

What is the state transition matrix for this new ecosystem where $\vec{x}[k] = \begin{bmatrix} \# \text{ of Herbivores}[k] \\ \# \text{ of Plants}[k] \\ \# \text{ of Babas}[k] \end{bmatrix}$?



- (b) If we start with 100 of each organism in the new ecosystem, how many organisms of each type will there be after an infinite number of time steps?

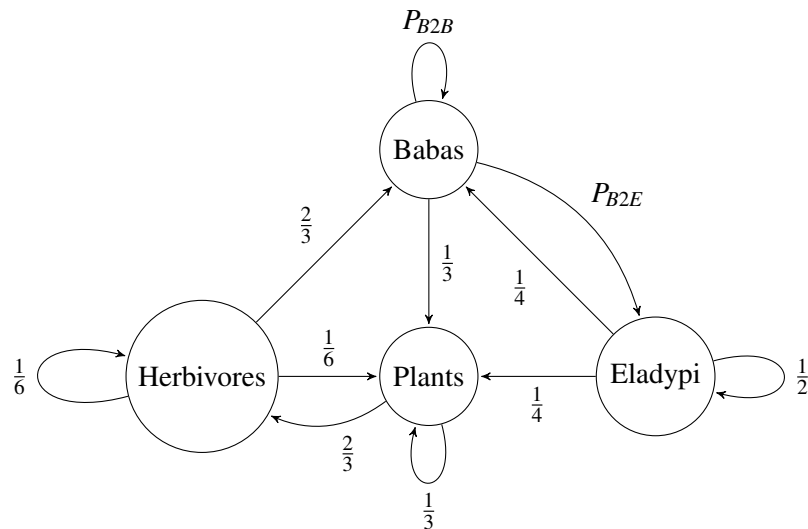- (c) After a few million years, an aquatic-based lifeform, the Eladypus, evolves a set of legs and enters the ecosystem. Having spent many years feasting on eels and sea snakes, the Eladypus has a diet restricted to Babas in this new environment. The new ecosystem can be modeled by the diagram shown below. Note that we don't know yet what fraction of the Babas is eaten by the Eladypi, but we will define that fraction as having a value of p_{B2E} (as indicated in the diagram). Given the rest of the constants indicated in the diagram below, as a function of p_{B2E} , what must be the value of p_{B2B} (i.e., at each time step, the fraction of Babas that remain in their current state)?



- (d) It's "Eladypi Week" on the Discovery Channel and we're hooked to the television trying to learn as much as we can about this unique creature. We learn that an ideal ecosystem has 350 Eladypi. Currently, we observe 600 Plants, 600 Herbivores, 300 Babas, and 400 Eladypi in our ecosystem. What is the fraction of Babas that the Eladypi can eat in order for the ecosystem to reach the ideal state after one transition? That is, what is the value of p_{B2E} that enables the ecosystem to reach the ideal state (in terms of the number of Eladypi) from its current state in one time step? With this value of p_{B2E} , how many Herbivores, Plants, and Babas are there after this single time step?

- (e) Given the value of p_{B2E} and the state (i.e., the number of Herbivores, Plants, Babas, and Eladypis after the single time step) you computed in part (d), will the number of Eladypi in the ecosystem remain constant after all future timesteps? You must mathematically justify your answer in order to receive credit for this problem.


8. Correlated Circuitry (20 pts)

In labs and homeworks you have been implementing `cross-correlation` in iPython and using helpful `numpy` functions such as `numpy.correlate` to calculate cross-correlation. This problem instead will guide you through designing a circuit that implements cross-correlation of an unknown input signal with a known signal.


- (a) Compute the cross correlation of $\vec{s}_1 = [3 \ 7]$ with respect to $\vec{s}_2 = [2 \ -3]$, where \vec{s}_1 and \vec{s}_2 are both periodic. Your output should be $\vec{y} = [y_0 \ y_1]$ where y_k corresponds to delaying \vec{s}_2 by k timesteps.
- (b) Now let's start designing a circuit that outputs the cross-correlation of an input signal \vec{v}_{in} with a known signal \vec{s} . Once again, the input signal $\vec{v}_{in}^T = [v_0 \ v_1]$ and the given signal $\vec{s}^T = [a \ b]$ are discrete signals with periods of **2**. The values of a and b are known, fixed and given to you, while the values of the input voltages v_0 and v_1 are unknown. Note that v_0 and v_1 can be treated as independent inputs to your design.

Draw a block diagram of a circuit that cross-correlates the input signal v_{in} with the given signal s and outputs the cross-correlation $\vec{y}^T = [y_0, y_1]$, with the outputs being defined the same way as they are in part (a).

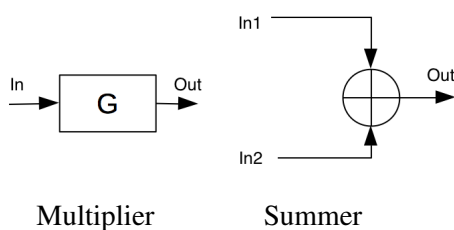Example diagrams for multipliers and summers are shown below to clarify what we mean by a block diagram for this problem.




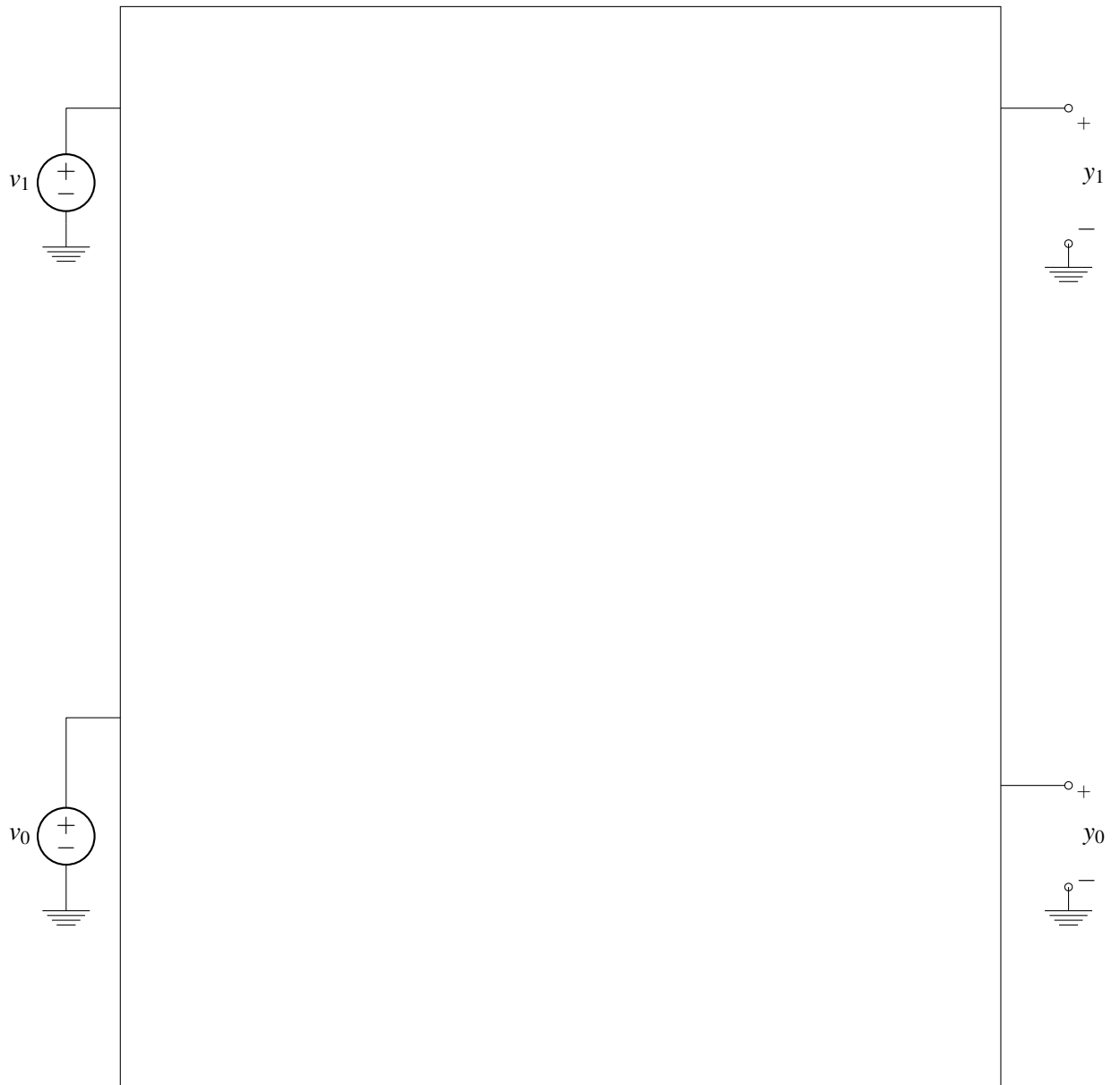- (c) Design a circuit that outputs the cross-correlation of $\vec{v}_{in}^T = [v_0 \ v_1]$ and $\vec{s}^T = [a \ b]$ for $a = -2$ and $b = -4$ using only **resistors** and **op amps**. Be sure to label your components and provide their values; your design must be drawn within the box below and use v_0 and v_1 as indicated.



- Note1: In this solution the scaling and summation are achieved in one stage. Other correct configurations involving a separation of scaling stage and summation stage are also acceptable, but they should always give a negative gain.
- Note2: It is not acceptable to simply join the outputs from the first stage directly together using just wires. Here is why: Take the circuit for y_0 as an example, the output of the one amplifier is $-2v_0$ and the output of the other amplifier is $-4v_0$. Unless $v_0 = 0$, these voltages are different. Now that you've connected these two outputs with a single wire, that means there is a voltage drop across this wire. This violates conservation of energy.

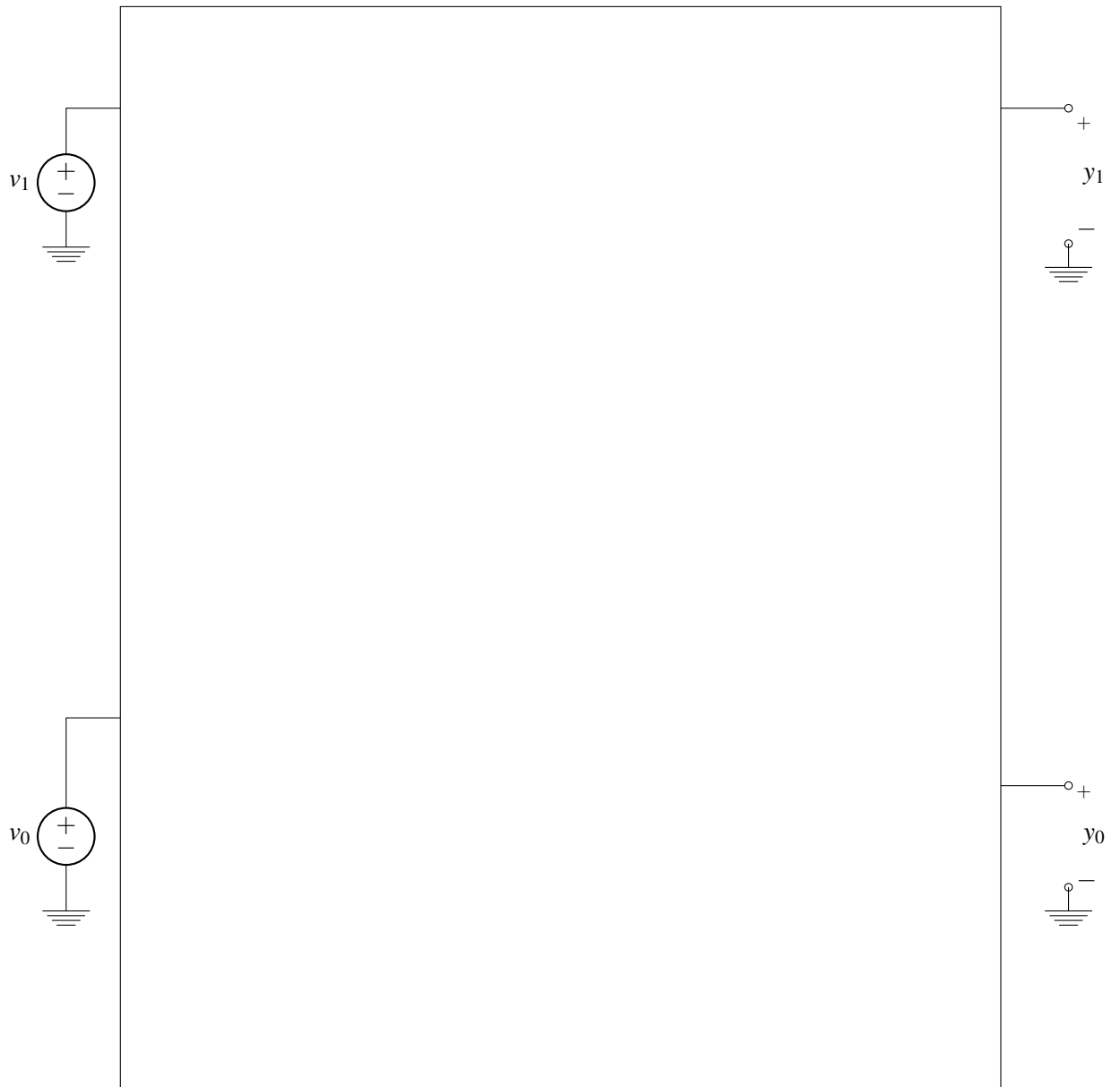- (d) Design a circuit that outputs the cross-correlation of $\vec{v}_{in}^T = [v_0 \ v_1]$ and $\vec{s}^T = [a \ b]$ for $a = 2$ and $b = 4$ using only **resistors** and **op amps**. Be sure to label your components and provide their values; your design must be drawn within the box below and use v_0 and v_1 as indicated.



- (e) **(BONUS: 5 pts)** Now let's assume that we want to be able to correlate v_{in} with respect to either $\vec{s}_1^T = [2 \ 4]$ or $\vec{s}_2^T = [-2 \ -4]$, where the choice between the two options is made by some external control signal(s). Using switches, blocks representing correct implementations of parts (c) and (d), and any additional resistors, sources, and op amps, design a circuit that would achieve this functionality. Be sure to label your components and provide their values.

9. Track This (20 pts)

In this question we will be working on a robot that must track an object moving along a straight path at an unknown but constant velocity. Specifically, the trajectory of the object is $y(t) = \alpha + \beta t$, where α is the unknown initial position of the object, and β is the unknown velocity of the object.

In general, our robot measures the position of the object at M time instants t_1, t_2, \dots, t_M . We denote our measurements by y_1, \dots, y_M . Unfortunately, our measurements are prone to error, caused by imperfections in our measurement instruments. What we therefore get is the following set of M expressions in two unknowns:

$$\alpha + t_1 \beta \approx y_1$$

$$\alpha + t_2 \beta \approx y_2$$

$$\vdots$$

$$\alpha + t_M \beta \approx y_M.$$

- (a) Rewrite the measurement expressions in matrix-vector form $\mathbf{A}\vec{x} \approx \vec{y}$, where $\vec{x}^T = [\alpha \ \beta]$.

(b) We know the least-squares solution to part (a) for $\hat{\vec{x}}$ is given by

$$\hat{\vec{x}} = \left(\mathbf{A}^T \mathbf{A} \right)^{-1} \mathbf{A}^T \vec{y}.$$

Determine a reasonably simple form for each of $\mathbf{A}^T \mathbf{A}$ and $\mathbf{A}^T \vec{y}$. Each of your expressions should be in terms of an appropriate subset of M , t_m , and y_m , where $m = 1, \dots, M$.

Note: Do NOT carry out the multiplication

$$\left(\mathbf{A}^T \mathbf{A} \right)^{-1} \mathbf{A}^T \vec{y}.$$

(c) Next we'll apply the Gram-Schmidt method to orthogonalize (but not orthonormalize) the columns of \mathbf{A} . Take as your first orthogonal vector $\vec{z}_1 = \vec{1}$ — that is, a vector of size M whose entries are all equal to 1. (Note that \vec{z}_1 does not have unit length, and we won't bother normalizing its length.)

Prove that each entry $z_{2,i}$ of the second orthogonal vector \vec{z}_2 is given by $z_{2,i} = t_i - \bar{t}$, where

$$\bar{t} = \frac{1}{M} \sum_{m=1}^M t_m.$$

Specifically, you must be sure to prove that \vec{z}_2 is in fact orthogonal to \vec{z}_1 .

- (d) Suppose we measure using a noisy apparatus the positions of the moving object at time instants $t_1 = 0$, $t_2 = 1$, and $t_3 = 5$ seconds, and that we've registered the following position values:

$$y(0) = 1, \quad y(1) = 3, \quad y(5) = 11.$$

Using the orthogonalization we developed in part (c), find the values of α and β that represent the line that best fits the measured data (in the least squared error sense).

PRINT your name and student ID: _____

10. Jumpbot Jumpbot Jumpbot (24 pts)

In this problem you will be designing circuits allowing a robot named Jumpbot to execute a set of commands that will be described below. Specifically, the output voltages produced by your circuits are interpreted by Jumpbot as setting its vertical position in meters.

Note that throughout this problem you must label all circuit component values, and that if you use any switches in your circuit, you must explain/note what voltage in your circuit would set the state of the switch to be open or closed. (In other words, you can't assume that switches will just be set to the appropriate state by some external signal at the appropriate time. Instead, your circuit must produce the control voltage for the switches.)


- (a) The first command we will design a circuit for is to enable Jumpbot to climb a ramp at a constant vertical rate of $20\frac{m}{s}$. Design a circuit that outputs a ramp voltage of slope $20\frac{V}{s}$. Label the output terminal V_{ramp} .

You can use only the following components in your design:


- Current Sources
- Voltage Sources
- Capacitors
- Resistors

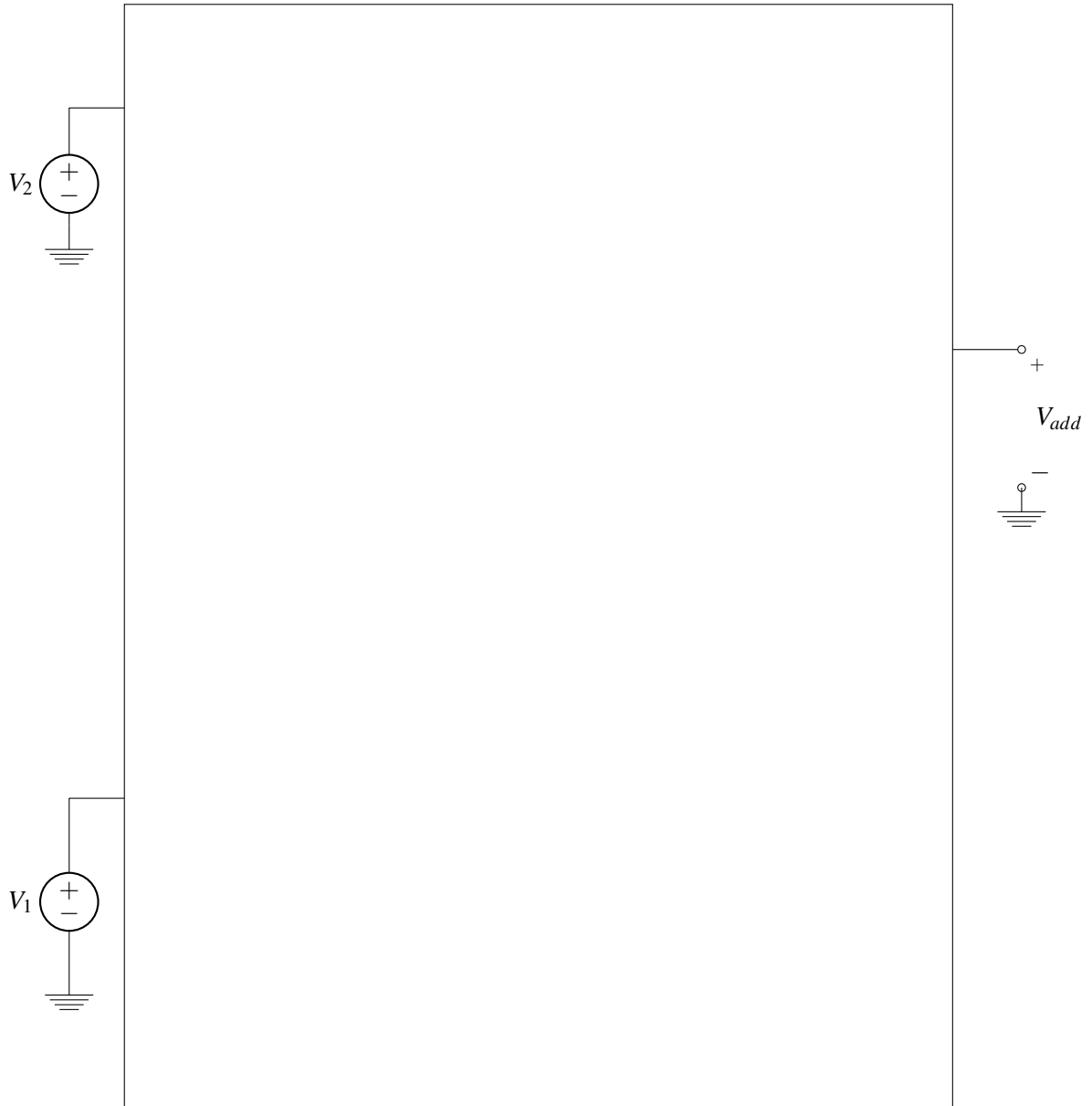- (b) Now we need to augment Jumpbot to perform the combination of two commands at once. Design a circuit that takes in two voltages (V_1 and V_2) and outputs $V_{add} = V_1 + V_2$. Your design must be drawn within the box below, and use V_1 and V_2 as indicated.

Your design for this circuit can use only op-amps and resistors.



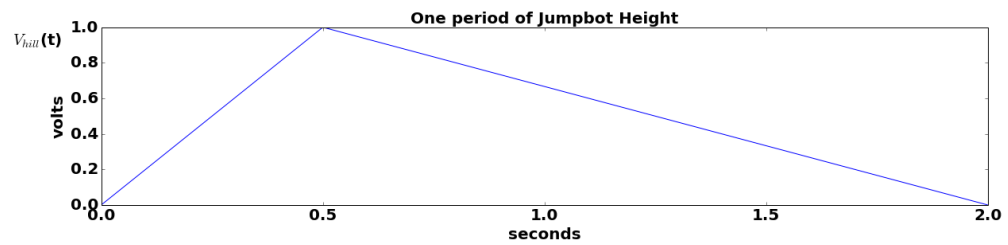- (c) Due to an issue with Jumpbot's mechanical design, he must take three times as long to go down a ramp as he does to go up one. Design a circuit that outputs the periodic $V_{hill}(t)$ shown below (note that two periods are shown in the figure) and that reflects this constraint.




For this design, you may use only the following components:

- Current Sources
- Voltage Sources
- Op-Amps
- Capacitors
- Resistors
- Switches

Note: You can complete the rest of this problem without having a correct design for this sub-part.

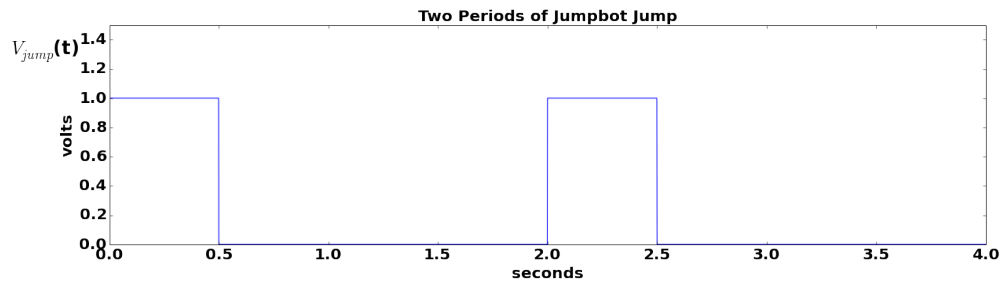- (d) Now let's allow Jumpbot to actually jump. His jumps occur with a periodicity of 2 seconds, and when he jumps, he immediately reaches a height of 1m for 0.5 seconds, after which he immediately returns to ground level.

Design a circuit that implements this jump command (two periods of which are shown below). Label your output terminal V_{jump} .



You can use only the following components in your design:

- Current Sources
- Voltage Sources
- Op-Amps
- Capacitors
- Resistors
- Switches
- A voltage source producing $V_{hill}(t)$ from part (c)

- (e) **(BONUS: 6 pts)** Design a circuit that would allow Jumpbot to climb a hill with a slope of $20 \frac{m}{s}$ while every 2 seconds also jumping over rocks that are 0.5m high, and that require him to be in the air for 0.5 seconds to clear the rocks.

You can use the following components for this design:

- Current Sources
- Voltage Sources
- Op-Amps
- Capacitors
- Resistors
- Switches
- A voltage source producing $V_{ramp}(t)$
- A voltage source producing $V_{jump}(t)$
- A correct implementation of the box from part (b)

PRINT your name and student ID: _____

- 11. Of Greedy Pursuits and Multipath Signals (22 pts)** In wireless communications, multipath propagation is the phenomenon in which a transmitted signal arrives at a receiver through two or more transmission paths—typically due to reflections from objects along the way.

Imagine a beacon that transmits a periodic discrete-time signal x . Each period of the signal is given by the vector

$$\vec{x} = \begin{bmatrix} x[0] \\ x[1] \\ x[2] \\ x[3] \\ x[4] \\ x[5] \\ x[6] \end{bmatrix} = \begin{bmatrix} 1 \\ 1 \\ 1 \\ -1 \\ -1 \\ 1 \\ -1 \end{bmatrix}$$

In other words, the transmitted signal has period 7, so $x[n+7] = x[n]$ for all integers n .

Recall that the autocorrelation function for a periodic signal \vec{x} is given by

$$R_{xx}[k] = \langle \vec{x}, \mathbf{S}^k \vec{x} \rangle = \vec{x}^T \mathbf{S}^k \vec{x},$$

where \mathbf{S} is the circular shift matrix:

$$\mathbf{S} = \begin{bmatrix} 0 & 0 & 0 & 0 & 0 & 0 & 1 \\ 1 & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 1 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 1 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 1 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 1 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 1 & 0 \end{bmatrix}$$

- (a) Determine the numerical value of $R_{xx}[0]$ and $R_{xx}[1]$.

For the remainder of this problem assume that the received signal y is a linear combination of delayed and scaled versions of the transmitted signal x . In particular, the received signal in vector form \vec{y} is given by:

$$\vec{y} = \alpha_L \mathbf{S}^L \vec{x} + \alpha_M \mathbf{S}^M \vec{x} = \alpha_L \vec{z}_L + \alpha_M \vec{z}_M, \quad (1)$$

where $\vec{z}_k = \mathbf{S}^k \vec{x}$ for $k = L, M$. Note that \vec{z}_k is the vector that represents one period of the k -sample delayed version of the transmitted signal x .

Let's now explore how to use OMP to determine the values of L and M as well as α_L and α_M from the received vector \vec{y} .

- (b) Assuming that $|R_{xx}[0]| \gg |R_{xx}[k]|$ for all $k \neq 0$, suggest an appropriate dictionary of vectors to use for OMP that will allow us to directly find L , M , α_L , and α_M . Explain in one to two sentences why you picked this dictionary.

Regardless of your answer to part (b), let's assume that you picked a dictionary of vectors consisting of the columns \vec{z}_i of the matrix $\mathbf{Z} = [\vec{z}_0 \ \vec{z}_1 \ \vec{z}_2 \ \vec{z}_3 \ \vec{z}_4 \ \vec{z}_5 \ \vec{z}_6]$ below:

$$\mathbf{Z} = \begin{bmatrix} 1 & -1 & 1 & -1 & -1 & 1 & 1 \\ 1 & 1 & -1 & 1 & -1 & -1 & 1 \\ 1 & 1 & 1 & -1 & 1 & -1 & -1 \\ -1 & 1 & 1 & 1 & -1 & 1 & -1 \\ -1 & -1 & 1 & 1 & 1 & -1 & 1 \\ 1 & -1 & -1 & 1 & 1 & 1 & -1 \\ -1 & 1 & -1 & -1 & 1 & 1 & 1 \end{bmatrix}$$

To save you some time in doing mechanical calculations, it is worth noting that the inner product of \vec{z}_i with \vec{z}_j is equal to 7 for $i = j$, and equal to -1 for $i \neq j$.

Finally, the received signal in vector form \vec{y} is:

$$\vec{y} = \begin{bmatrix} y[0] \\ y[1] \\ y[2] \\ y[3] \\ y[4] \\ y[5] \\ y[6] \end{bmatrix} = \begin{bmatrix} 1/2 \\ 3/2 \\ 3/2 \\ -1/2 \\ -3/2 \\ 1/2 \\ -1/2 \end{bmatrix}.$$

- (c) Now let's examine what happens during the first iteration of OMP. Assuming a Grunge-Fighting Oracle provides you with the information below, which column of \mathbf{Z} (i.e., which \vec{z}_i) will be selected? Given this choice, provide the expressions you would use to compute the residue signal at the end of the first iteration.

$$\vec{y}^T \mathbf{Z} = [\langle \vec{y}, \vec{z}_0 \rangle \quad \langle \vec{y}, \vec{z}_1 \rangle \quad \cdots \quad \langle \vec{y}, \vec{z}_6 \rangle] = \left[\frac{13}{2} \quad \frac{5}{2} \quad -\frac{3}{2} \quad -\frac{3}{2} \quad -\frac{3}{2} \quad -\frac{3}{2} \quad -\frac{3}{2} \right]$$

- (d) Now let's complete the second step of OMP, once again with the help of the Grunge-Fighting Oracle providing the information below. Note that the vector \vec{q}^T is the residue at the end of the first iteration. Which \vec{z}_i is selected in the second step? Finally, what are the values of L , M , α_L , and α_M ?

$$\underbrace{\begin{bmatrix} -\frac{3}{7} & \frac{4}{7} & \frac{4}{7} & \frac{3}{7} & -\frac{4}{7} & -\frac{3}{7} & \frac{3}{7} \end{bmatrix}}_{\vec{q}^T} \mathbf{Z} = [\langle \vec{q}, \vec{z}_0 \rangle \quad \langle \vec{q}, \vec{z}_1 \rangle \quad \cdots \quad \langle \vec{q}, \vec{z}_6 \rangle]$$

$$= \begin{bmatrix} 0 & \frac{24}{7} & -\frac{4}{7} & -\frac{4}{7} & -\frac{4}{7} & -\frac{4}{7} & -\frac{4}{7} \end{bmatrix}.$$

PRINT your name and student ID: _____

[If you are want the work on this page be graded, please state **CLEARLY** which problem(s) this space is for. You can also draw us something if you want or give us suggestions or complaints. You can also use this page to report anything suspicious that you might have noticed.]