

---

EECS 16A    Designing Information Devices and Systems I

Fall 2018

Homework 10

---

**You should plan to complete this homework by Thursday, November 1st. Everything in this homework is in scope for the midterm, but you do not need to turn anything in. There are no self-grades for this homework.**

## 1. Op-Amp in Negative Feedback

In this question, we are going to show that the second golden rule applies for op-amps in negative feedback. We will analyze circuits containing op-amps by first replacing the op-amp with our model, and then taking the limit as the open-loop gain ( $A$ ) approaches infinity.

Figure 1 shows the equivalent model of the op-amp. We can simplify further, by setting  $V_{DD} = -V_{SS}$  and assuming that the inputs ( $v_{in}$ ) are small enough for the output to not saturate to  $V_{DD}$  or  $V_{SS}$ . These assumptions result in the model in Figure 2 (Note 18, pg. 4).

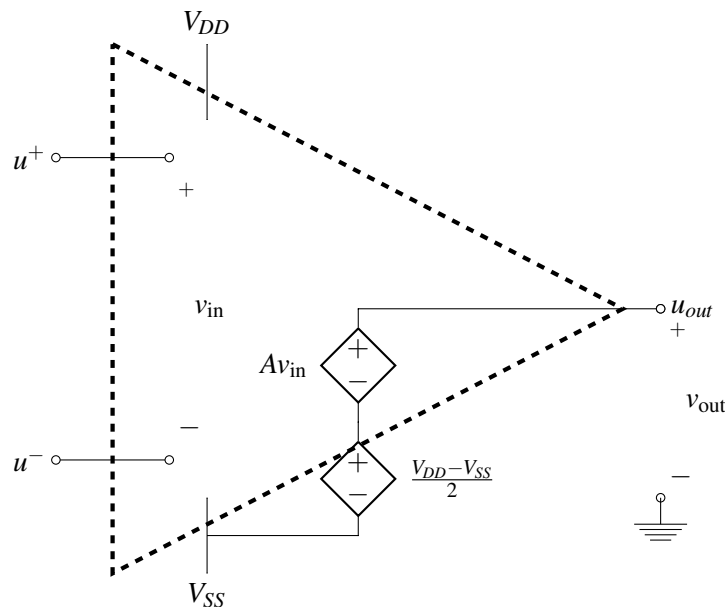


Figure 1: Op amp model


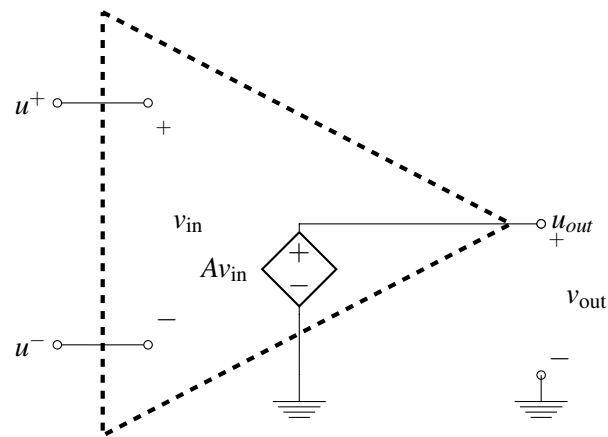


Figure 2: Op-amp model with the simplifying assumptions

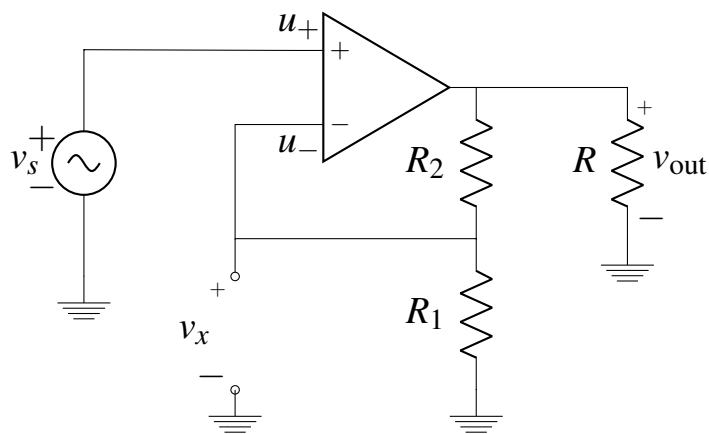
(a) Now consider the circuit below.

Draw an equivalent circuit by replacing the op-amp with the op-amp model shown above (Figure 2) and calculate  $v_{out}$  and  $v_x$  in terms of  $A$ ,  $v_s$ ,  $R_1$ ,  $R_2$  and  $R$ . Is the magnitude of  $v_x$  larger or smaller than the magnitude of  $v_s$ ? Do these values depend on  $R$ ?



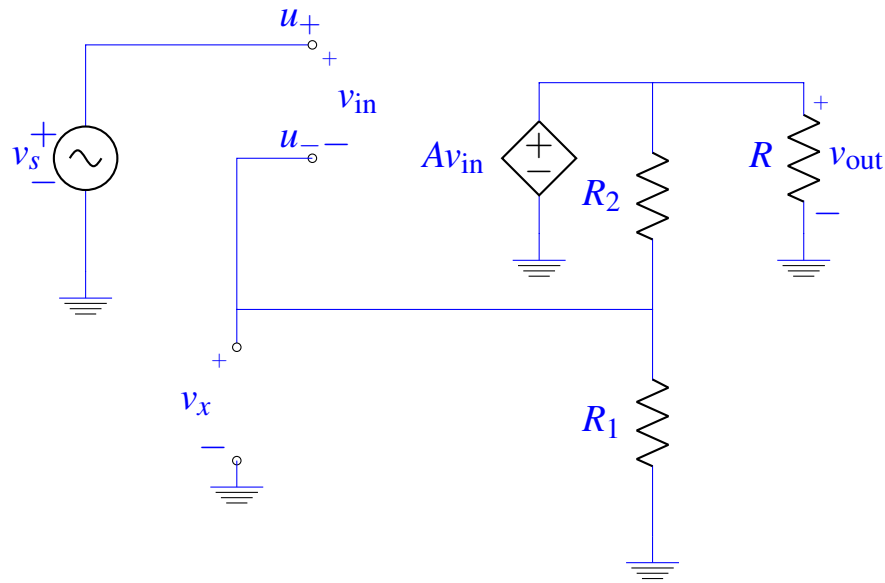**Solution:**

This is the equivalent circuit of the op-amp:



Since  $v_{out}$  is connected to the output of the op-amp, which is a voltage source, we can determine  $v_{out}$ :

$$\begin{aligned} v_{out} &= A(u_+ - u_-) \\ &= A(v_s - v_x) \end{aligned}$$

Since there is no current flowing into the op amp input terminals from nodes  $u_+$  and  $u_-$ ,  $R_1$  and  $R_2$  form a voltage divider and  $v_x = v_{out} \left( \frac{R_1}{R_1 + R_2} \right)$ . Thus, substituting and solving for  $v_{out}$ :

$$\begin{aligned} v_{out} &= A \left( v_s - v_{out} \frac{R_1}{R_1 + R_2} \right) \\ v_{out} &= v_s \left( \frac{1}{\frac{R_1}{R_1 + R_2} + \frac{1}{A}} \right) \end{aligned}$$

Knowing  $v_{out}$ , we can find  $v_x$ :

$$v_x = \frac{v_s}{1 + \frac{R_1 + R_2}{AR_1}}$$

Notice that  $v_x$  is slightly smaller than  $v_s$ , meaning that in equilibrium in the non-ideal case,  $v_+$  and  $v_-$  are not equal.  $v_{out}$  and  $v_x$  do not depend on  $R$ , which means that we can treat  $v_{out}$  as a voltage source that supplies a constant voltage independent of the load  $R$ .

- (b) Using your solution to part (a), calculate the limits of  $v_{\text{out}}$  and  $v_x$  as  $A \rightarrow \infty$ . Do you get the same answers if you apply the fact that  $u_+ = u_-$  when there is negative feedback?

**Solution:**

As  $A \rightarrow \infty$ , the fraction  $\frac{1}{A} \rightarrow 0$ , so

$$v_{\text{out}} = v_s \left( \frac{1}{\frac{R_1}{R_1 + R_2} + \frac{1}{A}} \right)$$

converges to

$$v_s \left( \frac{1}{\frac{R_1}{R_1 + R_2} + 0} \right) = v_s \left( \frac{R_1 + R_2}{R_1} \right).$$

Therefore, the limits as  $A \rightarrow \infty$  are:


$$v_{\text{out}} \rightarrow v_s \left( \frac{R_1 + R_2}{R_1} \right)$$

$$v_x \rightarrow v_s$$

If we observe the op amp is in negative feedback, we can apply the fact that  $u_+ = u_-$ . We get  $v_x = v_s$ . Then the current  $i$  flowing through  $R_1$  to ground is  $\frac{v_s}{R_1}$ . By KCL, this same current flows through  $R_2$  since no current flows into the negative input terminal of the op amp ( $u_-$ ). Thus, the voltage drop across  $R_2$  is  $v_{\text{out}} - v_x = i \cdot R_2 = v_s \left( \frac{R_2}{R_1} \right)$ . Therefore,  $v_{\text{out}} = v_s + v_s \left( \frac{R_2}{R_1} \right) = v_s \left( \frac{R_1 + R_2}{R_1} \right)$ . The answers are the same if you take the limit as  $A \rightarrow \infty$ .

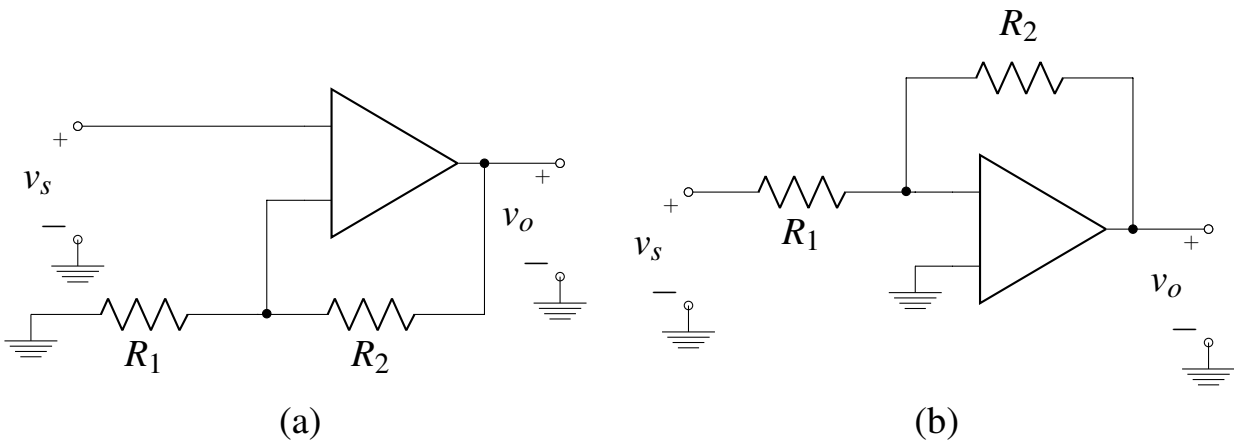
## 2. Basic Amplifier Building Blocks

The following amplifier stages are used often in many circuits and are well known as (a) the non-inverting amplifier and (b) the inverting amplifier.



- (a) Label the input terminals of the op-amp labeled (a), so that it is in negative feedback. Then derive the voltage gain ( $A_v = \frac{v_o}{v_s}$ ) of the non-inverting amplifier using the Golden Rules. Explain the origin of the name of the amplifier.

**Solution:**

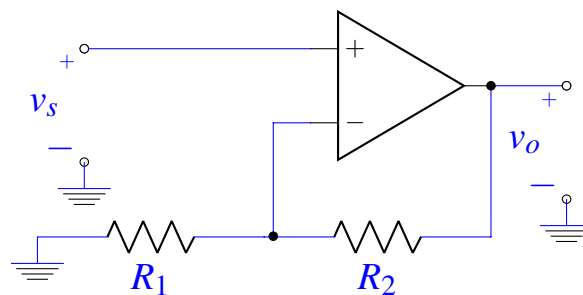

The  $+$ ,  $-$  should be labeled on the top and bottom of the op amp, respectively. There are many ways to solve these circuits; here are some:

**Method 1:** The voltage at the positive input terminal is  $v_s$ , so by the Golden Rules, the op-amp will act such that the voltage at the negative input terminal also becomes  $v_s$ . Therefore, the voltage drop across  $R_1$  is  $v_s$ , so there is a current of  $i = \frac{v_s}{R_1}$  through resistor  $R_1$ . Since no current flows into the negative input terminal (by the Golden Rules), this current of  $i$  must flow through  $R_2$  (by KCL at the inverting input). Thus, the voltage drop across  $R_2$  is  $V_2 = i \cdot R_2 = v_s \left( \frac{R_2}{R_1} \right)$ . Therefore,  $v_o$  is  $v_s$  plus the voltage drop across  $R_2$ :

$$v_o = v_s + v_s \left( \frac{R_2}{R_1} \right) = v_s \left( \frac{R_1 + R_2}{R_1} \right)$$

**Method 2:** Since there is no current flowing into the negative input terminal (by the Golden Rules), notice that the resistors  $R_1$  and  $R_2$  form a voltage di-

vider between the output  $v_o$  and ground. The negative input terminal sees the output of this voltage divider:

$$u_- = v_o \left( \frac{R_1}{R_1 + R_2} \right)$$

But  $u_- = u_+ = v_s$  by the Golden Rules, so we have:

$$v_o \left( \frac{R_1}{R_1 + R_2} \right) = v_s \implies v_o = v_s \left( \frac{R_1 + R_2}{R_1} \right)$$


Therefore, the gain of this amplifier is:

$$A_v = \frac{v_o}{v_s} = \frac{R_1 + R_2}{R_1}$$

This is called an *non-inverting amplifier* because the gain  $A_v$  is positive – it does not invert the input signal (in contrast to the amplifier in the next part of this problem).

- (b) Label the input terminals of the op-amp labeled (b), so that it is negative feedback. Then derive the voltage gain ( $A_v = \frac{v_o}{v_s}$ ) of the inverting amplifier using the Golden Rules. Explain the origin of the name of the amplifier.

**Solution:**

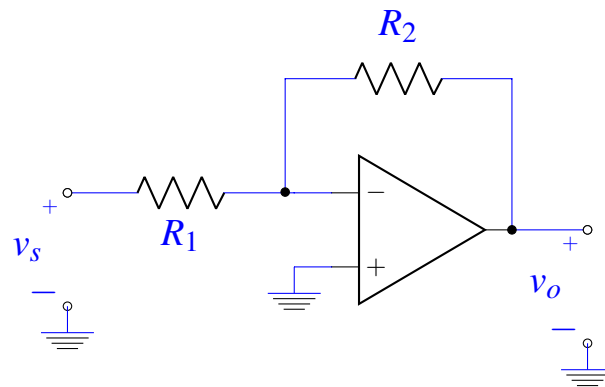

The  $+$ ,  $-$  should be labelled on the bottom and top of the op amp, respectively. Here is one way to solve for the gain:

Since the potential at the positive input terminal is  $u_+ = 0$ , the op-amp will act such that the potential at the negative input terminal is  $u_- = 0$  as well (by the Golden Rules). Now, by KCL at the node with potential  $u_-$ :

$$\frac{v_s - 0}{R_1} + \frac{v_o - 0}{R_2} = 0$$

Solving this yields:

$$v_o = - \left( \frac{R_2}{R_1} \right) v_s$$

Thus, the voltage gain of this amplifier circuit is:

$$A_v = \frac{v_o}{v_s} = - \frac{R_2}{R_1}$$

This is called an *inverting amplifier* because the voltage gain  $A_v$  is *negative*, meaning it “inverts” its input signal.

### 3. Cool For The Summer


You and a friend want to make a box that helps control an air conditioning unit. You both have dials that display a voltage: 0 means that you want to leave the temperature as it is. Negative voltages mean that you want to reduce the temperature. (It’s hot, so we will assume that you never want to increase the temperature – so, we’re not talking about a Berkeley summer...)

Your air conditioning unit, however, responds to positive voltages. The higher the magnitude of the voltage, the stronger it runs. At zero, it is off.

Therefore, you need a box that is an inverting summer – it outputs a weighted sum of two voltages where the weights are both negative. The sum is weighted because each of you has your own subjective sense of how much to turn the dial down, so you need to compensate for this.

This problem walks you through this using an op-amp.

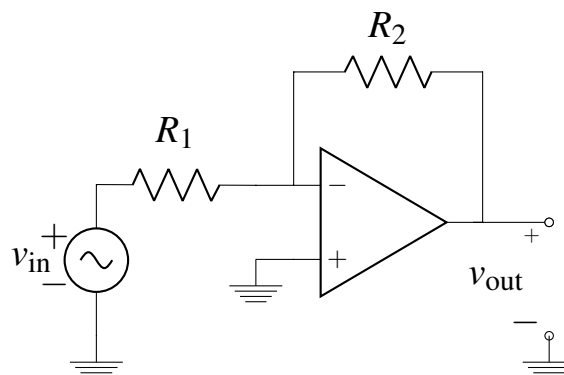(a) As a first step, find  $v_{\text{out}}$  in terms of  $R_2$ ,  $R_1$ ,  $v_{\text{in}}$ .



**Solution:** First, we need to check that the amplifier is in negative feedback. In other words, if the negative input terminal is moved upward, the feedback needs to move it back downward. Going around the loop:

- We move the negative input of the op amp upward
- The output of the amplifier moves downward
- The negative input moves downward with it

The important thing here is that the result of the initial stimulus needs to go in the opposite direction of the initial stimulus! Thus, we've confirmed that the amplifier is in negative feedback.

Second, we perform KCL.

$$\frac{v_{in} - u_-}{R_1} + \frac{v_{out} - u_-}{R_2} = 0$$


Since we're in negative feedback, we can apply the golden rules. From those, we know the voltages at the negative and positive input terminals of the amplifier— $u_-$  and  $u_+$ , respectively—are held at the same voltage. In other words,  $u_+ = u_- = 0V$ .

$$\frac{v_{in}}{R_1} + \frac{v_{out}}{R_2} = 0$$

$$v_{out} = v_{in} \left( -\frac{R_2}{R_1} \right)$$

The general inverting amplifier shown above has a voltage gain  $v_{out} = -\frac{R_2}{R_1}v_{in}$ .

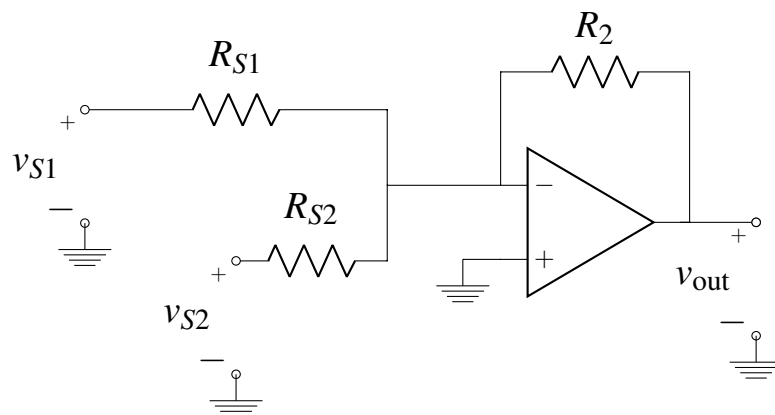- (b) Now we will add a second input to this circuit as shown below. Find  $v_{out}$  in terms of  $v_{S1}$ ,  $v_{S2}$ ,  $R_{S1}$ ,  $R_{S2}$  and  $R_2$ .



**Solution:**

Method 1: Superposition



We can find the overall voltage gain of this amplifier using superposition. When  $v_{S1}$  is on, we can ignore  $R_{S2}$ . From the Golden Rules, we know that the voltage at the  $-$  terminal of the op-amp must be equal to the voltage at the  $+$  terminal. Thus, the voltage across  $R_{S2}$  is 0V. Now apply the equation from part (a)  $v_{\text{out}} = -\frac{R_2}{R_{S1}}v_{S1}$ . Similarly, when  $v_{S2}$  is on, we get  $v_{\text{out}} = -\frac{R_2}{R_{S2}}v_{S2}$ . Combining the two equations, we get  $v_{\text{out}} = -R_2 \left( \frac{v_{S1}}{R_{S1}} + \frac{v_{S2}}{R_{S2}} \right)$ .

### Method 2: KCL without superposition

The following analysis is also correct and arrives at the same conclusion. According to the golden rules,  $u_- = u_+ = 0\text{V}$ , so we can write a single equation and solve:

$$\frac{v_{S1}}{R_{S1}} + \frac{v_{S2}}{R_{S2}} + \frac{v_{\text{out}}}{R_2} = 0$$

$$v_{\text{out}} = -v_{S1} \left( \frac{R_2}{R_{S1}} \right) - v_{S2} \left( \frac{R_2}{R_{S2}} \right)$$

- (c) Let's suppose that you want  $v_{\text{out}} = -\left(\frac{1}{4}v_{S1} + 2v_{S2}\right)$  where  $v_{S1}$  and  $v_{S2}$  represent the input voltages from you and your friend. Select resistor values such that the circuit implements this desired relationship.


**Solution:** Using the configuration from the previous part, the conditions which need to be satisfied are:

- $\frac{R_2}{R_{S1}} = \frac{1}{4}$
- $\frac{R_2}{R_{S2}} = 2$

One possible set of values is  $R_2 = 2\text{k}\Omega$ ,  $R_{S1} = 8\text{k}\Omega$ , and  $R_{S2} = 1\text{k}\Omega$ , but any combination of resistors which satisfies the conditions listed above are valid solutions.

- (d) Now suppose that you have another AC unit that you want to add to the same room. This unit however, functions opposite to the already existing unit; it responds to negative voltages. You want to run both units at the same time. Add another op-amp based circuit to the circuit in part (b), so that you invert the output of the circuit from part (b).

**Solution:**

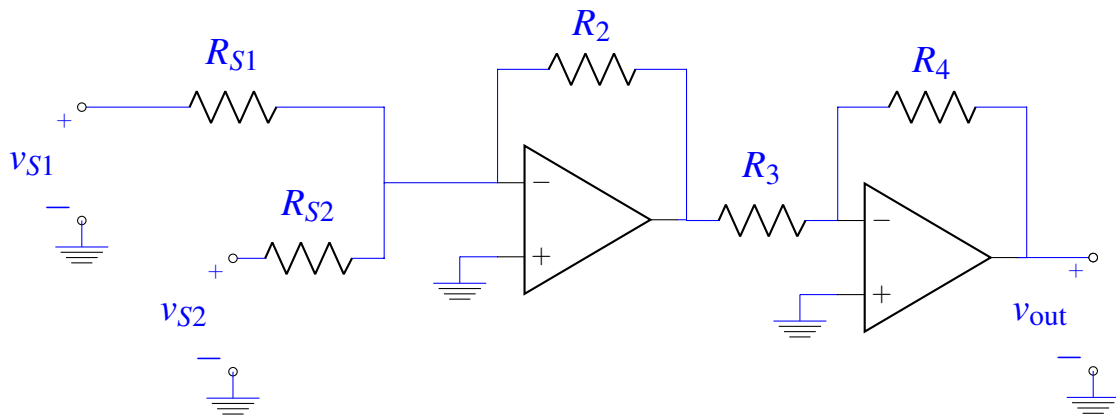

Here, we add another inverting op-amp stage with a voltage gain of 1, and we can pick any equal-valued resistors for  $R_3$  and  $R_4$ .

#### 4. Island Karaoke Machine

You're stuck on a desert island and everyone is bored out of their minds. Fortunately, you have your EE16A lab kit with op-amps, wires, resistors, and your handy breadboard. You decide to build a karaoke machine. You recover one speaker from the crash remains and use your iPhone as your source. You know that many songs put instruments on either the "left" or the "right" channel, but the vocals are usually present on both channels with equal strength.


The Thevenin equivalent model of the iPhone audio jack and speakers is shown below. We assume that the audio signals  $v_{\text{left}}$  and  $v_{\text{right}}$  have equivalent source resistance of the left/right audio channels of  $R_{\text{left}} = R_{\text{right}} = 3\Omega$ . The speaker has an equivalent resistance of  $R_{\text{speaker}} = 4\Omega$ .

For this problem, we'll assume that the vocals are present on both left and right channels, but the instruments are only present on the right channel, i.e.


$$\begin{aligned} v_{\text{left}} &= v_{\text{vocals}} \\ v_{\text{right}} &= v_{\text{vocals}} + v_{\text{instrument}}, \end{aligned}$$

where the voltage source  $v_{\text{vocals}}$  can have values anywhere in the range of  $\pm 120\text{mV}$  and  $v_{\text{instrument}}$  can have values anywhere in the range of  $\pm 50\text{mV}$ .

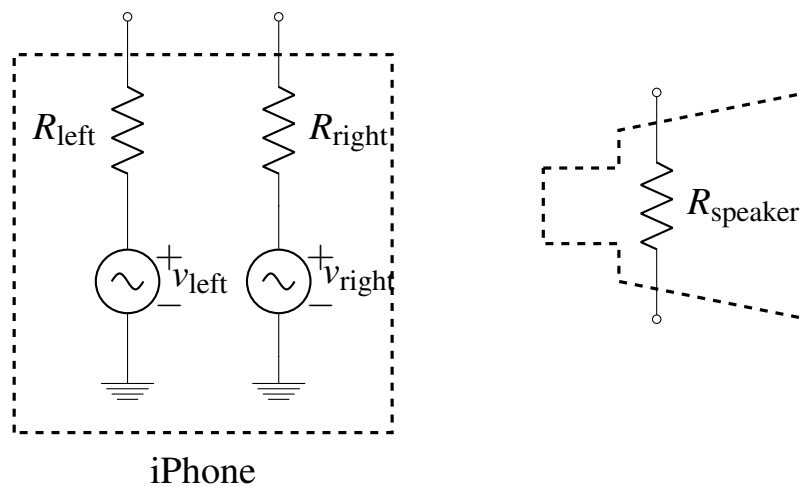What is the goal of a karaoke machine? The ultimate goal is to *remove* the vocals from the audio output. We're going to do this by first building a circuit that takes the left and right audio outputs of the smartphone and then calculates its difference. Let's see what happens.




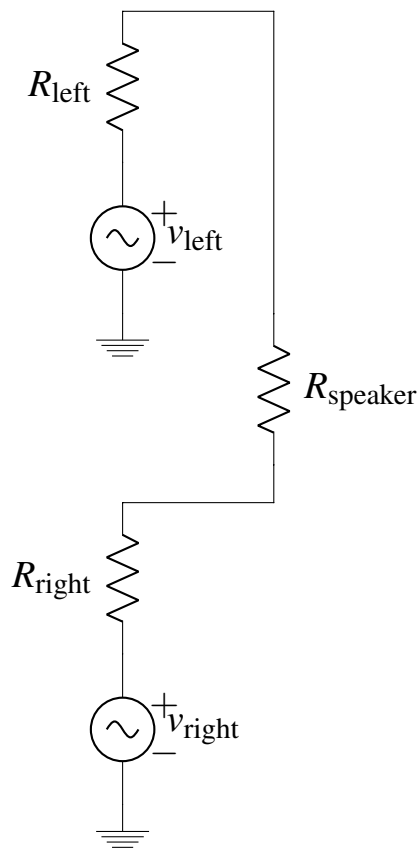- (a) One of your island survivors suggests the following circuit to do this. Calculate the voltage across the speaker as a function of  $v_{\text{vocals}}$  and  $v_{\text{instruments}}$ . Does the voltage across the speaker depend on  $v_{\text{vocals}}$ ? What do you think the islanders will hear – vocals, instruments, or both?



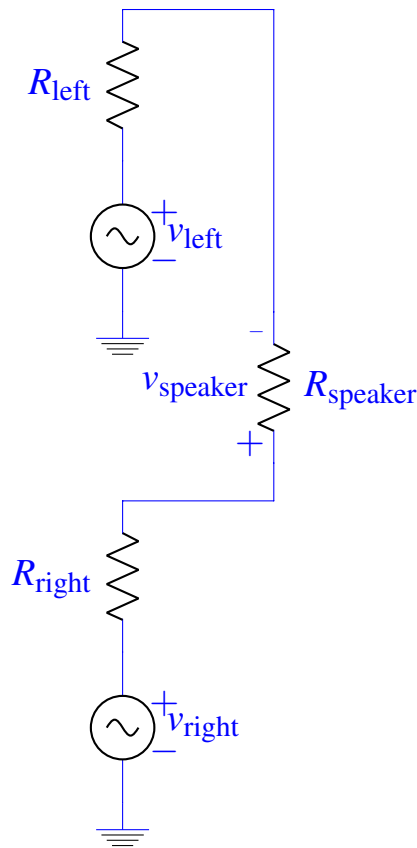**Solution:**

Let's mark the voltage across the speaker,  $v_{\text{speaker}}$ , from bottom to top as in the figure:



We can apply the principle of superposition to solve for  $v_{\text{speaker}}$ . First, we solve for the voltage across the speaker when only  $v_{\text{left}}$  is on. Let's call this  $v_{\text{speaker, left}}$ . Notice that the circuit becomes a voltage divider. Therefore, we get

$$-v_{\text{speaker, left}} = \frac{v_{\text{left}} R_{\text{speaker}}}{R_{\text{speaker}} + R_{\text{left}} + R_{\text{right}}} = \frac{4v_{\text{vocals}}}{10} = 0.4v_{\text{vocals}},$$

giving

$$v_{\text{speaker, left}} = -0.4v_{\text{vocals}}.$$

Similarly, we solve for the voltage across the speaker when only  $v_{\text{right}}$  is on. Let's call this  $v_{\text{speaker, right}}$ . Again, notice that the circuit becomes a voltage divider. Therefore, we get

$$v_{\text{speaker, right}} = \frac{v_{\text{right}} R_{\text{speaker}}}{R_{\text{speaker}} + R_{\text{left}} + R_{\text{right}}} = \frac{4(v_{\text{vocals}} + v_{\text{instrument}})}{10} = 0.4(v_{\text{vocals}} + v_{\text{instrument}}).$$

Superposition tells us that  $v_{\text{speaker}} = v_{\text{speaker, left}} + v_{\text{speaker, right}} = 0.4v_{\text{instrument}} = 0.4 \cdot 50 \text{ mV} = 20 \text{ mV}$ .

What did you notice? The vocals got canceled out! The islanders will only hear the instruments, just as they wanted.

- (b) We need to boost the sound level to get the party going. We can do this by *amplifying* both  $v_{\text{left}}$  and  $v_{\text{right}}$ . Keep in mind that we could use inverting or non-inverting amplifiers.


Let's assume, just for this part, that we have already implemented circuits that amplify  $v_{\text{left}}$  and  $v_{\text{right}}$  by some factor  $A_v$  (Consider  $A_v = 100$  for this part). We now have two voltages,  $v_{\text{G1}}$  and  $v_{\text{G2}}$  that are  $A_v \cdot v_{\text{left}}$  and  $A_v \cdot v_{\text{right}}$  respectively. Use  $v_{\text{G1}}$  and  $v_{\text{G2}}$  to get  $A_v \cdot v_{\text{instrument}}$  across  $R_{\text{speaker}}$ .

**Solution:**


**Note:** In the following figures, we use a symbolic representation of the amplifier with gain  $A_v = 100$ . We will add in the corresponding amplifier circuit in part c.

We have three components of the circuit we want to build that we already know:

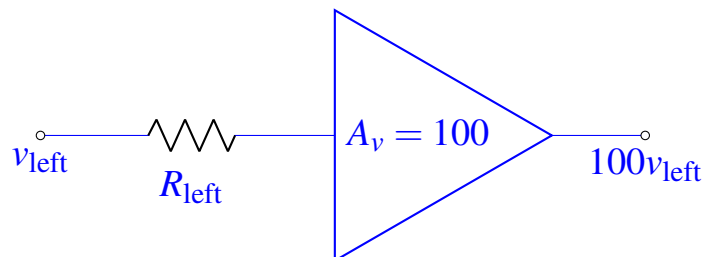- The part of the circuit that amplifies  $v_{\text{left}}$  to  $100v_{\text{left}}$ , which we can draw as below:




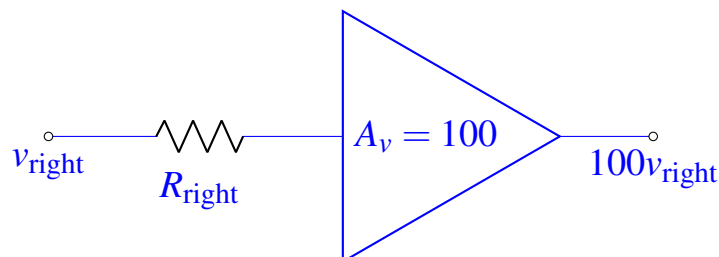- The part of the circuit that amplifies  $v_{\text{right}}$  to  $100v_{\text{right}}$ , which we can draw as below:



- The speaker

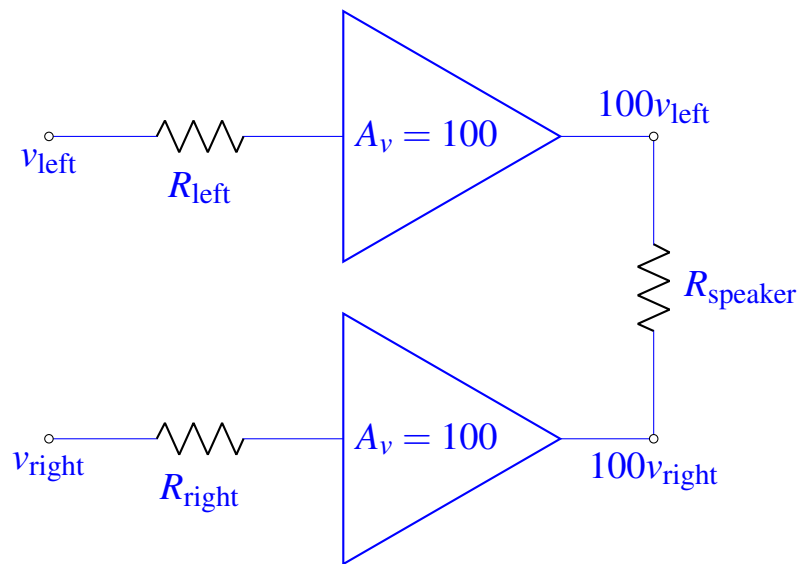If we want to take the difference of the two amplified outputs across the speaker, all we need to do is connect the output terminals of the first two components to the terminals of the speaker as shown below:



You can see this solution taking inspiration from part (a). Why do we get exactly  $100(v_{\text{right}} - v_{\text{left}})$  across the speaker? Why does the voltage not divide as before?

To answer this, look back at the circuit for the non-inverting amplifier. If we solve for the Thevenin output resistance of this circuit, we will find that it is zero. Furthermore, the Thevenin voltage will be  $100v_{\text{left}}$  (or  $100v_{\text{right}}$ ). This implies that, no matter what  $R_{\text{left}}$  or  $R_{\text{right}}$  is, we are going to only see  $100v_{\text{left}}$  or  $100v_{\text{right}}$  at the output.

- (c) Now, you want  $\pm 2\text{V}$  across the speaker to get the party going. Using the scheme in part (b), design a circuit that takes in  $v_{\text{left}}$  and  $v_{\text{right}}$  and outputs an amplified version of  $v_{\text{instrument}}$  across the speaker with the range of  $\pm 2\text{V}$ . You need to design both amplifiers with the right gain  $A_v$  to achieve this.

You can use up to two op-amps, and each of them can be inverting or non-inverting.


### Solution:

Feed the non-ideal voltage source  $\{v_{\text{left}}, R_{\text{left}}\}$  into a non-inverting amplifier with gain  $A_v$  and the non-ideal voltage  $\{v_{\text{right}}, R_{\text{right}}\}$  into another non inverting amplifier with gain  $A_v$ . (We have a different gain from the previous part, which we need to determine.) Then connect the two outputs across  $R_{\text{speaker}}$  as shown in the previous part.

In this circuit, we will get  $v_{\text{speaker}} = A_v \cdot v_{\text{instrument}}$ . Since  $v_{\text{instrument}}$  has a range of  $\pm 50\text{mV}$ ,  $v_{\text{speaker}}$  will have a range of  $\pm 50\text{mV} \cdot A_v = \pm 0.05 \cdot A_v \text{V}$ . Now we need  $\pm 0.05 \cdot A_v \text{V} = \pm 2$ , i.e.  $A_v = 40$ .

Therefore, we want to design a non-inverting amplifier with voltage gain of 40.

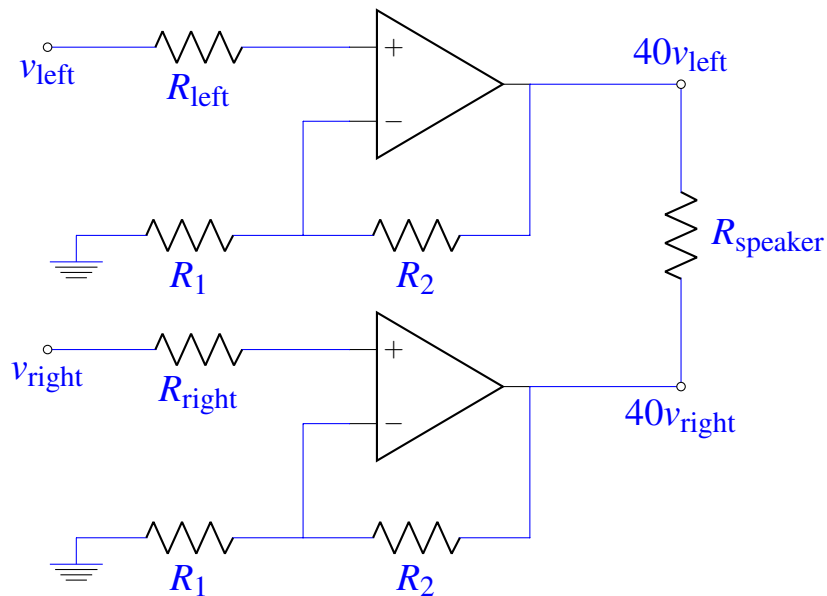We can use the circuit schematic from part (b), but now, we just need to design the non-inverting amplifier with op-amps to have gain 40. We get the equivalent circuit below:




Now, we need to find  $R_1$  and  $R_2$ .

$$A_v = 1 + \frac{R_2}{R_1}$$

Therefore, we can then choose any  $R_1$  and  $R_2$  such that  $\frac{R_2}{R_1} = 39$ . Note that there are multiple ways of choosing them. One such choice is  $R_1 = 1\text{ k}\Omega$  and  $R_2 = 39\text{ k}\Omega$ , for instance.

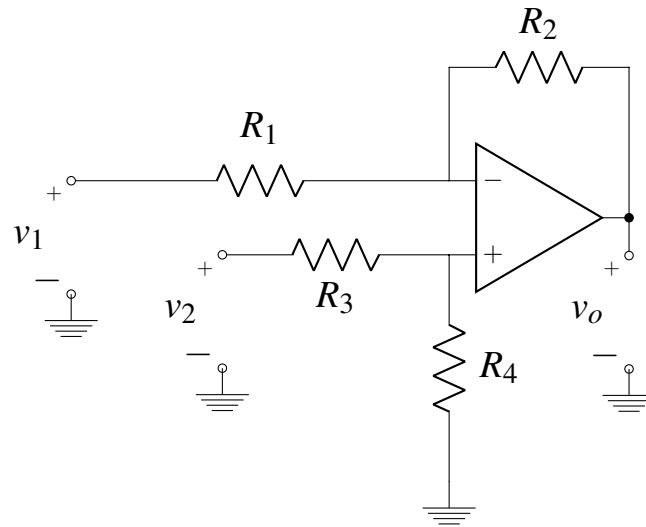- (d) The trouble with the approach in part (c) is that multiple op-amps are required. Let's say you only have one op-amp with you. What would you do? One night in your dreams, you have an inspiration. Why not combine the inverting and non-inverting amplifier into one, as shown below!



If we set  $v_2 = 0\text{ V}$ , what is the output  $v_o$  in terms of  $v_1$ ? (This is the inverting path.)

**Solution:**

If we set  $v_2 = 0\text{ V}$ , we would get  $u_+ = 0\text{ V}$ . Applying the Golden Rules, we will get  $u_- = u_+ = 0\text{ V}$ . Writing KCL at the  $-$  terminal of the op-amp, we get

$$\frac{v_1 - 0}{R_1} = \frac{0 - v_{o,1}}{R_2},$$

which gives

$$v_{o,1} = \frac{-v_1 R_2}{R_1}.$$

(e) If we set  $v_1 = 0\text{ V}$ , what is the output  $v_o$  in terms of  $v_2$ ? (This is the non-inverting path.)

**Solution:**

If we set  $v_1 = 0\text{ V}$ , we would get  $u_+ = \frac{v_2 R_4}{R_3 + R_4} = u_-$ . Writing KCL at the  $-$  terminal gives

$$\frac{0 - u_-}{R_1} = \frac{u_- - v_{o,2}}{R_2},$$

which gives

$$v_{o,2} = u_- \left( 1 + \frac{R_2}{R_1} \right) = v_2 \left( \frac{R_4}{R_3 + R_4} \right) \left( 1 + \frac{R_2}{R_1} \right).$$

(f) Now, determine  $v_o$  in terms of  $v_1$  and  $v_2$ . (*Hint:* Use superposition.) Choose values for  $R_1$ ,  $R_2$ ,  $R_3$  and  $R_4$ , such that the speaker has  $\pm 2\text{ V}$  across it.



**Solution:**

By the principle of superposition,

$$v_o = v_{o,1} + v_{o,2}.$$

If we set  $v_1 = v_{\text{left}}$  and  $v_2 = v_{\text{right}}$ , we'd ideally want  $v_o = -40v_1 + 40v_2$ . We can choose  $R_1$ ,  $R_2$ ,  $R_3$  and  $R_4$ , so that this happens.

How do we do this? Let's do this in steps. First, note that, looking for the expression for  $v_{o,1}$ , we'll want  $\frac{R_2}{R_1} = 40$ . Therefore, we can choose any values of  $R_2$  and  $R_1$ , such that this happens. One such choice is  $R_1 = 1 \text{ k}\Omega$  and  $R_2 = 40 \text{ k}\Omega$ . Then, plug that into the expression of  $v_{o,2}$ , and the condition we now want is

$$\left( \frac{R_4}{R_3 + R_4} \right) \left( 1 + \frac{R_2}{R_1} \right) = 40,$$

which gives us

$$\frac{R_4}{R_3 + R_4} = \frac{40}{41}.$$

Thus, we need to choose  $R_3$  and  $R_4$ . As before, we can choose these values in many ways. One such choice is  $R_4 = 40 \text{ k}\Omega$  and  $R_3 = 1 \text{ k}\Omega$ .

**Note:** Keep in mind that, for this problem, we actually assumed that  $v_1 = v_{\text{left}}$  and  $v_2 = v_{\text{right}}$ , which would mean that we are ideally connecting  $v_{\text{left}}$  and  $v_{\text{right}}$  as inputs. However, in reality, we're actually connecting the outputs from the iPhone as inputs. This means that  $R_{\text{left}}$  and  $R_{\text{right}}$  will also actually affect the output.

With this effect, we will actually get

$$v_o = -\frac{v_1 R_2}{R_{1,eq}} + v_2 \left( \frac{R_4}{R_{3,eq} + R_4} \right) \left( 1 + \frac{R_2}{R_{1,eq}} \right),$$

where  $R_{1,eq} = R_1 + R_{\text{left}}$  and  $R_{3,eq} = R_3 + R_{\text{right}}$ .


Therefore, we can just *fold in* the effect of  $R_{\text{left}}$  and  $R_{\text{right}}$  into these. For instance, we want to set  $R_{3,eq} = 1 \text{ k}\Omega$ . Now, we can actually make  $R_3 = R_{3,eq} - 3 \Omega = 997 \Omega$  and  $R_1 = R_{1,eq} - 3 \Omega = 997 \Omega$ .

Give yourself full credit even if you didn't notice this, but keep this in mind!


*Bonus:* Can you now see why we wanted to keep  $R_1$  and  $R_3$  in the order of  $\text{k}\Omega$  or larger?
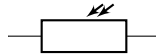
## 5. PetBot Design

In this problem, you will design circuits to control PetBot, a simple robot designed to follow light. PetBot measures light using photoresistors. A photoresistor is a light-sensitive resistor. As it is exposed to more light, its resistance decreases. Given below is the circuit symbol for a photoresistor.



Below is the basic layout of the PetBot. It has one motor on each wheel. We will model each motor as a  $1\ \Omega$  resistor. When motors have positive voltage across them, they drive forward; when they have negative voltage across them, they drive backward. At zero voltage across the motors, the PetBot stops. The speed of the motor is directly proportional to the magnitude of the motor voltage. The light sensor is mounted to the front of the robot.

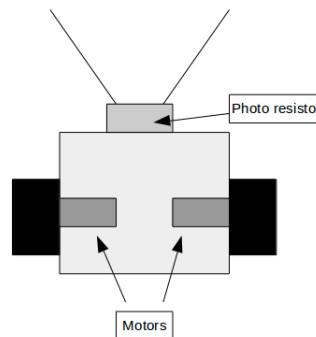

- (a) **Speed control** – Let us begin by first having PetBot decrease its speed as it drives toward the flashlight.


Design a motor driver circuit that outputs a decreasing positive motor voltage as the PetBot drives toward the flashlight. The motor voltage should be at least  $5\text{ V}$  far away from the flashlight. When far away from the flashlight, the photoresistor value will be  $10\text{ k}\Omega$  and dropping toward  $100\ \Omega$  as it gets closer to the flashlight.

In your design, you may use any number of resistors and just 1 op-amp. You also have access to voltage sources of  $10\text{ V}$  and  $-10\text{ V}$ . Based on your circuit, derive an expression for the motor voltage as a function of the circuit components that you used.

**Hint:** You should consider the loading effect of connecting this circuit to your motor, which has resistance. A buffer may help solve this problem.

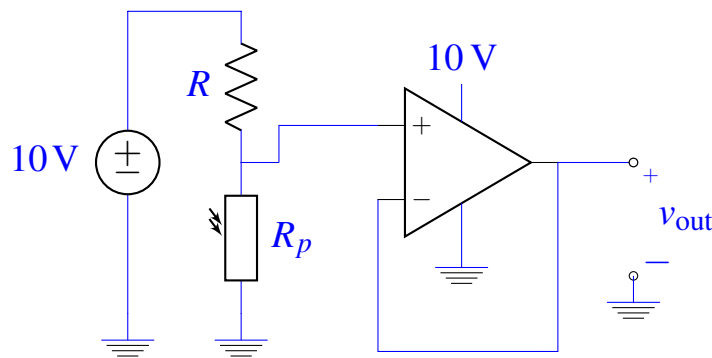**Solution:**

We can use a voltage divider circuit to adjust the output motor voltage as the PetBot drives towards the flashlight (and the photoresistor's resistance decreases).



The output of the above circuit is:

$$v_{\text{out}} = \frac{R_p}{R_p + R} \cdot 10 \text{ V}$$

where  $R_p$  represents the photoresistor. Note that we use a voltage buffer to prevent loading effects when connecting the motor.

We set  $R \leq 10 \text{ k}\Omega$  to achieve  $v_{\text{out}} \geq 5 \text{ V}$  when the PetBot is far away from the flashlight (i.e.  $R_p = 10 \text{ k}\Omega$ ). As the PetBot drives towards the flashlight, the resistance  $R_p$  drops, so that  $v_{\text{out}}$ , the motor voltage, decreases.


- (b) **Distance control** – Let us now have PetBot drive up to a flashlight (or away from the flashlight) and stop at distance of 1 m away from the light. At the distance of 1 m from the flashlight, the photoresistor has a value  $1 \text{ k}\Omega$ .

Design a circuit to output a motor voltage that is positive when the PetBot is at a distance greater than 1 m from the flashlight (making the PetBot move toward it), zero at 1 m from the flashlight (making the PetBot stop), and negative at a distance of less than 1 m from the flashlight (making the PetBot back away from the flashlight.)

In your design, you may use any number of resistors and just 1 op-amp. You also have access to voltage sources of  $10 \text{ V}$  and  $-10 \text{ V}$ . Based on your circuit, derive an expression for the motor voltage as a function of the values of circuit components that you used.

**Solution:**

We outline two possible solutions here:

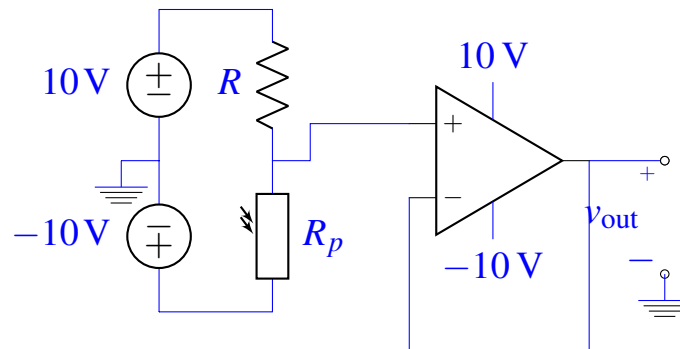
**Method 1:**

Here observe that  $v_{\text{out}} = u_+$ . Using superposition we find that

$$v_{\text{out}} = u_+ = 10 \frac{R_p}{R + R_p} - 10 \frac{R}{R + R_p} = 10 \frac{R_p - R}{R + R_p}$$

To satisfy the condition that  $v_{\text{out}} = 0$  when Petbot is 1 m away, we have that  $R = 1 \text{ k}\Omega$ . Similar to the previous design, we can do the analysis for when the Petbot is far away and close by. We will show how to do it when the Petbot is close by here.

$$\begin{aligned} R_p &< R = 1 \text{ k}\Omega \\ \Rightarrow R_p - R &< 0 \\ \Rightarrow v_{\text{out}} &= 10 \frac{R - R_p}{R + R_p} < 0 \end{aligned}$$

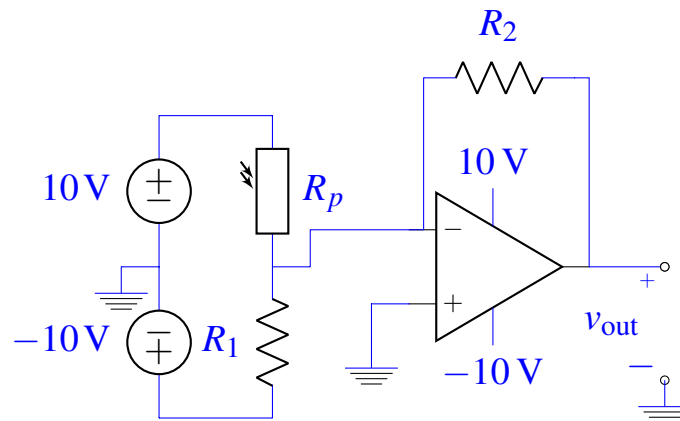**Method 2:**

Choosing  $R_1 = R = 1 \text{ k}\Omega$  we observe that the voltage  $v_{\text{out}} = 0$  when Petbot is 1 m away as required. To find  $v_{\text{out}}$  more generally, observe that  $u_- = u_+ = 0$ , so we need to find the current  $i$  going through  $R_2$  from node  $u_-$  to node  $u_{\text{out}}$  to get  $v_{\text{out}}$ .

$$v_{\text{out}} = -iR_2 = -\left(\frac{10}{R_p} + \frac{-10}{R_1}\right)R_2$$

From this we see that when PetBot is greater than 1 m away we have

$$\begin{aligned} R_p &> R_1 = 1 \text{ k}\Omega \\ \frac{1}{R_p} - \frac{1}{R_1} &< 0 \\ \Rightarrow -\left(\frac{1}{R_p} - \frac{1}{R_1}\right) \cdot 10R_2 &> 0 \end{aligned}$$

Similarly when the Petbot is less than 1 m away, we have that the motor voltage will be negative.

## 6. Homework Process and Study Group

Who else did you work with on this homework? List names and student ID's. (In case of homework party, you can also just describe the group.) How did you work on this homework?

### Solution:

I worked on this homework with...

I first worked by myself for 2 hours, but got stuck on problem 5, so I went to office hours on...

Then I went to homework party for a few hours, where I finished the homework.