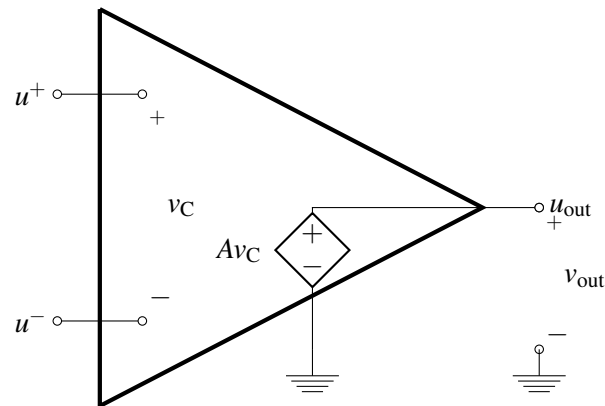

EECS 16A
Fall 2018

Designing Information Devices and Systems I

Discussion 9B

1. Op-Amp Golden Rules

Here is an equivalent circuit of an op-amp (where we are assuming that $V_{SS} = -V_{DD}$) for reference:



- (a) What are the currents flowing into the positive and negative terminals of the op-amp (i.e., what are I^+ and I^-)? What are some of the advantages of your answer with respect to using an op-amp in your circuit designs?

Answer:


The u^+ and u^- terminals have no closed circuit connection between them, and therefore no current can flow into or out of them. This is very good because we can connect an op-amp to any other circuit, and the op-amp will not disturb that circuit in any way because it does not load the circuit (it is an open circuit).

- (b) Suppose we add a resistor of value R_L between u_{out} and ground. What is the value of v_{out} ? Does your answer depend on R_L ? In other words, how does R_L affect Av_C ? What are the implications of this with respect to using op-amps in circuit design?

Answer:

Notice that u_{out} is connected directly to a controlled/dependent voltage source, and therefore v_{out} will always have to be equal to Av_C regardless of what R_L is connected to the op-amp. This is very advantageous because it means that the output of the op-amp can be connected to any other circuit (except a voltage source), and we will always get the desired/expected voltage out of the op-amp.

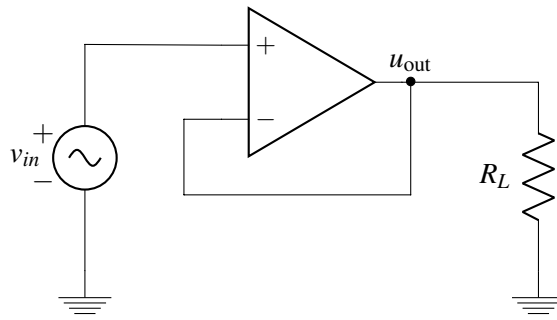For the rest of the problem, consider the following op-amp circuit in negative feedback:



- (c) Assuming that this is an ideal op-amp, what is v_{out} ?

Answer:

Recall for an ideal op-amp in negative feedback, we know from the Golden Rules that $u^+ = u^-$. In this case, $u^- = u_{out} = u^+$.

- (d) Draw the equivalent circuit for this op-amp and calculate v_{out} in terms of A , v_{in} , and R_L for the circuit in negative feedback. Does v_{out} depend on R_L ? What is v_{out} in the limit as $A \rightarrow \infty$?


Answer:

Notice that the op-amp can be modeled as a voltage-controlled voltage source. Thus, we have the following equation:

$$\begin{aligned} v_{out} &= A(v_{in} - v_{out}) \\ v_{out} + Av_{out} &= Av_{in} \\ v_{out} &= v_{in} \frac{A}{1+A} \end{aligned}$$

Thus, as $A \rightarrow \infty$, $v_{out} \rightarrow v_{in}$. This is the same as what we get after applying the op-amp Golden Rules. Notice that output voltage does not depend on R . Thus, this circuit acts like a voltage source that provides the same voltage read at u^+ without drawing any current from the terminal at u^+ . This is why the circuit is often referred to as a “unity gain buffer,” “voltage follower,” or just “buffer.”

2. A Trans-Resistance Amplifier

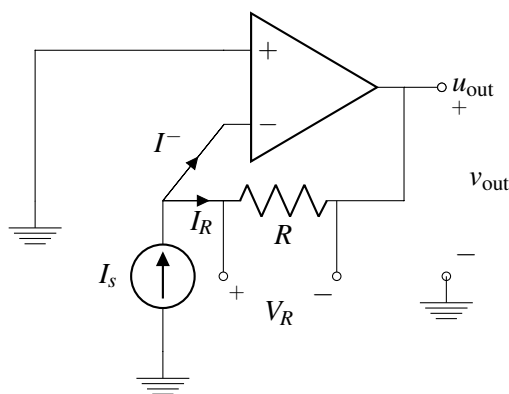

- (a) Use the Golden Rules to calculate v_{out} as a function of I_s and R .


Answer:

$I^- = 0$, so $I_s = I_R$. Thus, $V_R = I_s R$.

Using Golden Rules, $u^- = 0$ V, and thus $v_{out} = u^- - V_R = -I_s R$.

- (b) Use the Golden Rules to implement the same behavior as the above circuit (with a current source), but use a voltage source and a resistor instead.


Answer:

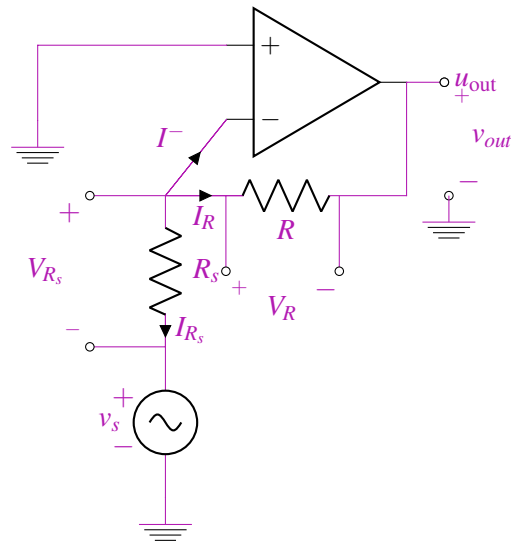

Remember, $u^- = 0\text{ V}$ because of the Golden Rules. Applying KCL and the Golden Rules, we see that $I_{R_s} + I_R = 0 \Rightarrow I_{R_s} = -I_R$. In addition, applying Ohm's Law, $I_{R_s} = -\frac{v_s}{R_s}$, so $I_R = \frac{v_s}{R_s}$.

Hence, $v_{out} = -V_R = -\frac{v_s}{R_s} R = -\frac{R}{R_s} v_s$. This is the **inverting amplifier**.


3. Multiple Inputs To One Op-Amp

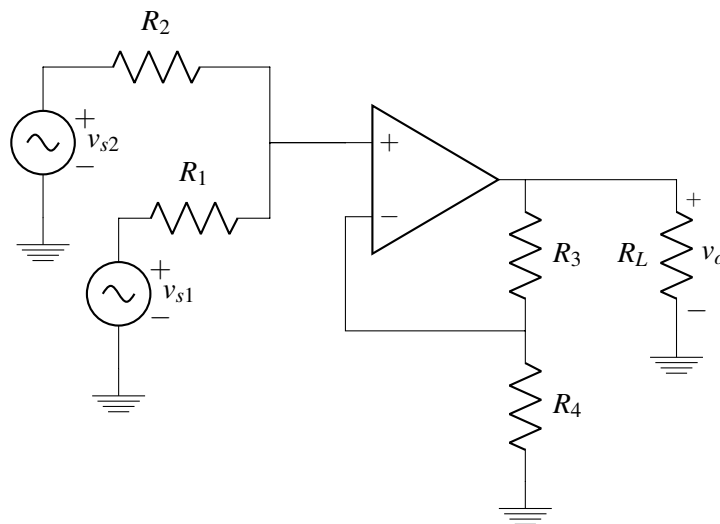

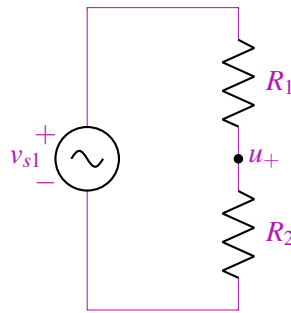- (a) For the circuit above, find an expression for v_o . (Hint: Use superposition.)

Answer:


Let's call the potential at the positive input of the op-amp u_+ . Using superposition, we first turn off v_{s2} and find u_+ . The circuit then looks like:



We recognize the above circuit as a voltage divider. Thus,

$$u_{+,vs1} = \frac{R_2}{R_1 + R_2} v_{s1}$$

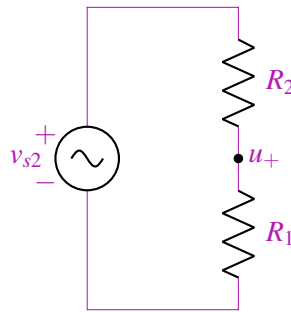By symmetry, we expect v_{s2} to have a similar circuit and expression. The circuit for v_{s2} looks like:



The expression for u_+ with v_{s2} is then:

$$u_{+,vs2} = \frac{R_1}{R_1 + R_2} v_{s2}$$

From superposition, we know the output must be the sum of these.

$$u_+ = \frac{R_2}{R_1 + R_2} v_{s1} + \frac{R_1}{R_1 + R_2} v_{s2}$$

With u_+ determined, we can find the output voltage directly from the formula for a non-inverting amplifier. We can also derive it using the process below.

From the Golden Rules, $u_+ = u_-$. Using voltage dividers, we can express u_- in terms of v_o :

$$u_- = \frac{R_4}{R_3 + R_4} v_o$$

$$v_o = \left(1 + \frac{R_3}{R_4}\right) u_- = \left(1 + \frac{R_3}{R_4}\right) u_+$$

Now, to find the final output, we can set u_+ to our earlier expression.

$$v_o = \left(1 + \frac{R_3}{R_4}\right) \left(\frac{R_2}{R_1 + R_2} v_{s1} + \frac{R_1}{R_1 + R_2} v_{s2} \right)$$

- (b) How could you use this circuit to find the sum of different signals?


Answer:

The circuit already finds the weighted sum of two inputs. By setting $R_1 = R_2$ and $R_3 = R_4$, we can take the exact sum of two inputs.

$$v_o = \left(1 + \frac{R_3}{R_4}\right) \left(\frac{R_2}{R_1 + R_2} v_{s1} + \frac{R_1}{R_1 + R_2} v_{s2}\right) = (1 + 1) \left(\frac{1}{2} v_{s1} + \frac{1}{2} v_{s2}\right) = v_{s1} + v_{s2}$$

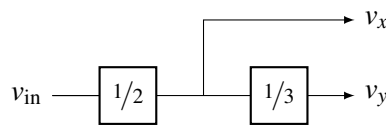4. Modular Circuits

In this problem, we will explore the design of circuits that perform a set of (arbitrary) mathematical operations in order to elucidate some of the important properties and uses of op-amps in negative feedback. In the last discussion, we noticed that voltage dividers are not compose-able, so we will use op-amps instead. Again, recall that we want to implement the block diagram shown below:




In other words, we want to implement a circuit with two outputs v_x and v_y , where $v_x = \frac{1}{2} v_{in}$ and $v_y = \frac{1}{3} v_x$.

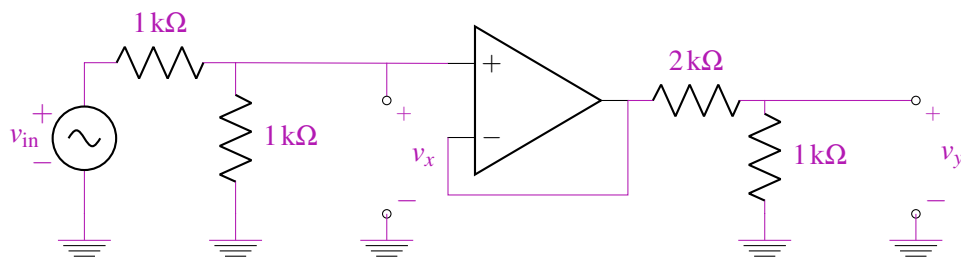- (a) Using an ideal op-amp in negative feedback, modify the design of one of the two voltage divider circuits you built (i.e. the $\frac{1}{2}$ block or the $\frac{1}{3}$ block), so that the originally intended relationships between v_x and v_{in} as well as v_y and v_x are realized by the resulting overall circuit (where each block is replaced by its individual implementation). Is this configuration enough by itself to attach loads at v_x and v_y ?

Answer:

Use a voltage buffer. Note that this configuration's outputs would change with the addition of a load. As a follow-up, think about ways to make the outputs agnostic to the loads attached. If we used the latter half of the circuit as a fractional divider block, we would need to buffer the output.





- (b) Now let's assume that we want to expand our toolbox of circuits that implement mathematical operations. In particular, design blocks that implement:
- $v_o = 5 v_i$
 - $v_o = -2 v_i$
 - $v_o = v_{i1} + v_{i2}$



Pay careful attention to the way you design these blocks, so that connecting any one block to any other block does not modify the intended functionality of any of the blocks.

Answer:



i.

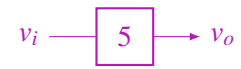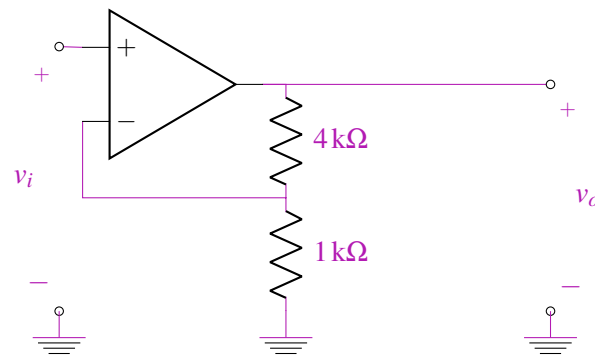


ii.

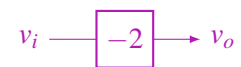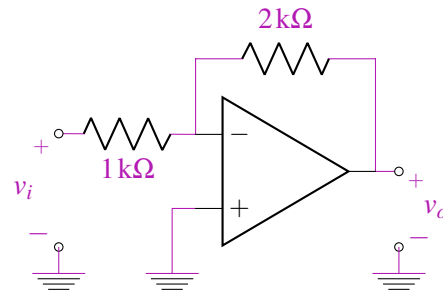

iii.

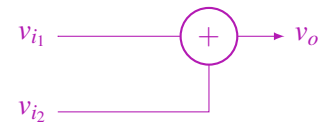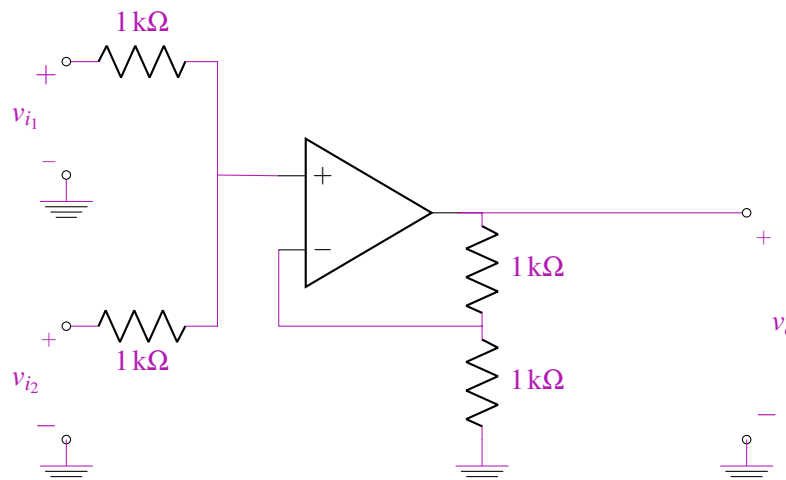

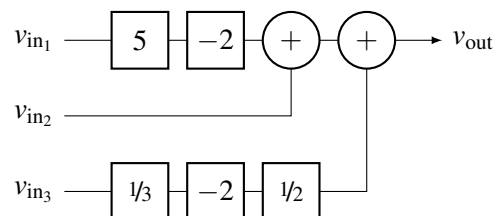(c) Check that your designs from part (b) indeed enable a library of compose-able elements (i.e., that you can connect any block to any other block without having the intended functionality be modified) by implementing the block diagram shown below.



Answer:

If op-amps are used properly to drive the output of each stage, there will be no load on any stage due

to the previous stage. This will give us the behavior we want. We get:

$$v_{\text{out}} = -10v_{\text{in}_1} + v_{\text{in}_2} - \frac{1}{3}v_{\text{in}_3}$$