

### 3. Fruity Fred

$$(a) R_{AB} = \rho \frac{L-kF}{A_c} + \rho \frac{L-kF}{A_c} = \frac{2\rho(L-kF)}{A_c}$$

$$(b) F = \frac{A_c V_{out} + 2\rho L(V_{out} - 1)}{2\rho k(V_{out} - 1)}$$

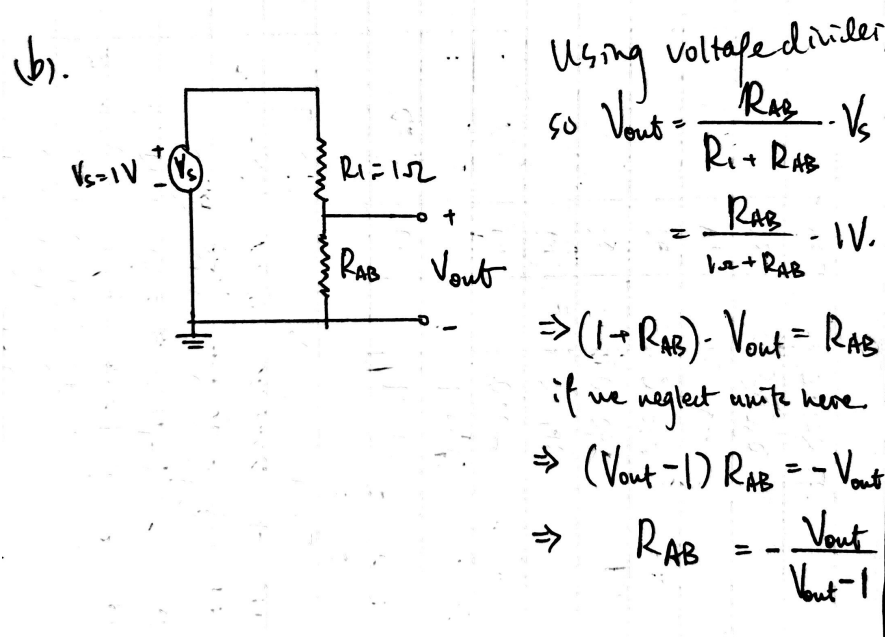


Figure 1: Circuit Designed

As deduced from the process on the picture, so  $R_{AB} = -\frac{V_{out}}{V_{out} - 1}$ . Also, as we derived from part (a), which gives  $R_{AB} = \frac{2\rho(L-kF)}{A_c}$ . Thus, we have that:

$$\begin{aligned} R_{AB} &= \frac{2\rho(L-kF)}{A_c} = -\frac{V_{out}}{V_{out} - 1} \\ \Rightarrow 2\rho(L-kF) \cdot -(V_{out} - 1) &= A_c \cdot V_{out} \\ \Rightarrow (2\rho L - 2\rho kF) \cdot -(V_{out} - 1) &= A_c \cdot V_{out} \\ \Rightarrow -2\rho L(V_{out} - 1) + 2\rho k(V_{out} - 1)F &= A_c \cdot V_{out} \\ \Rightarrow 2\rho k(V_{out} - 1)F &= A_c \cdot V_{out} + 2\rho L(V_{out} - 1) \\ \Rightarrow F &= \frac{A_c V_{out} + 2\rho L(V_{out} - 1)}{2\rho k(V_{out} - 1)} \end{aligned}$$