

1 Double-Check Your Intuition

(a) $8.85 \cdot 10^{-12} F/m \cdot \frac{L_{\text{train}}W}{h}$ for both capacitances

Since $\epsilon_{\text{air}} = 8.85 \cdot 10^{-12} F/m$, so we have that $C = \epsilon \frac{A}{d} = 8.85 \cdot 10^{-12} F/m \cdot \frac{L_{\text{train}}W}{h}$

This is the capacitance between both T_1 , M and T_2 , M

Parts (b), (c), and more explanation/graph of (d) on the next page. Below is just the concluded equation for $V_{C_{eq}}(t)$ for more clarity.

(d) Equation:

$$V_{C_{eq}}(t) = \text{when } k\tau \leq t \leq (k+\frac{1}{2})\tau, \text{ then } \frac{I_1}{C_{eq}}(t-k\tau); \text{ when } (k+\frac{1}{2})\tau < t < (k+1)\tau, \text{ then } -\frac{I_1}{C_{eq}}(t-k\tau-\frac{\tau}{2}) + \frac{I_1\tau}{2C_{eq}}$$


1. Maglev.

(b) C_{T1} C_{T2} They're connected to each other in series.

(c) $C_{eq} = C_{T1} \parallel C_{T2} = \frac{C_{T1} C_{T2}}{C_{T1} + C_{T2}} = \frac{C_{T1}^2}{2 C_{T1}}$ with $C_{T1} = C_{T2} \neq 0$, so cancelling.

Thus, $C_{eq} = \frac{C_{T1}}{2} = \left[4.425 \cdot 10^{-12} \text{ F/m} \cdot \frac{L_{\text{train}} \cdot W}{h} \right]$

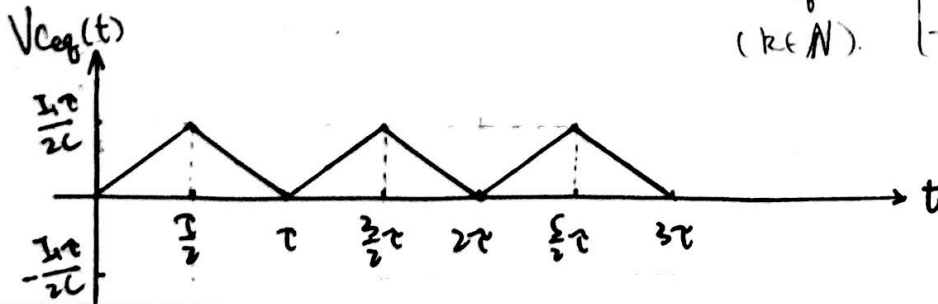
(d) Since at $t=0$, $V_{eq}(0) = 0V$, and when a constant current source is applied, we have $V_{eq}(t) = \frac{1}{C} t + V_{eq}(0)$, and since I_s is constant from $t=0$ to $t = \frac{\tau}{2}$, so $V_{eq}(t) = \frac{1}{C} t$ for $t \in [0, \frac{\tau}{2}]$. Using similar logic as Note 17, we have $V_{eq}(t) = \frac{1}{C} (t - t_0) + V_{eq}(t_0)$ and so here we supply each period ($\frac{\tau}{2}$) of constant current, so the voltage pattern mimics the one on the note 17, and thus is: $V_{eq}(t) = \begin{cases} \frac{I_s}{C_{eq}} (t - k\tau) & \text{when } k\tau \leq t \leq (k + \frac{1}{2})\tau \\ -\frac{I_s}{C_{eq}} (t - k\tau - \frac{\tau}{2}) + \frac{I_s \tau}{2C_{eq}} & \text{when } (k + \frac{1}{2})\tau \leq t \leq (k+1)\tau \end{cases}$ ($k \in \mathbb{N}$).




(c). When $d < 1\text{ cm}$ then $C_{eq} = 4.425 \cdot 10^{-12} \text{ F/m} \cdot \frac{L_{train} \cdot w}{d} \geq 4.425 \cdot 10^{-12} \text{ F/m} \cdot \frac{100\text{m} \cdot 1\text{cm}}{1\text{cm}}$
 with $L_{train} = 100\text{m}$, $w = 1\text{cm}$, so, $C_{eq} \geq 4.425 \cdot 10^{-10} \text{ F}$.

Thus, $V_{Ceq} \leq \frac{I_s \tau}{2C_{eq}} < \frac{1\text{mA} \cdot 1\mu\text{s}}{2 \cdot 4.425 \cdot 10^{-10} \text{ F}} = 1.13 \text{ V}$

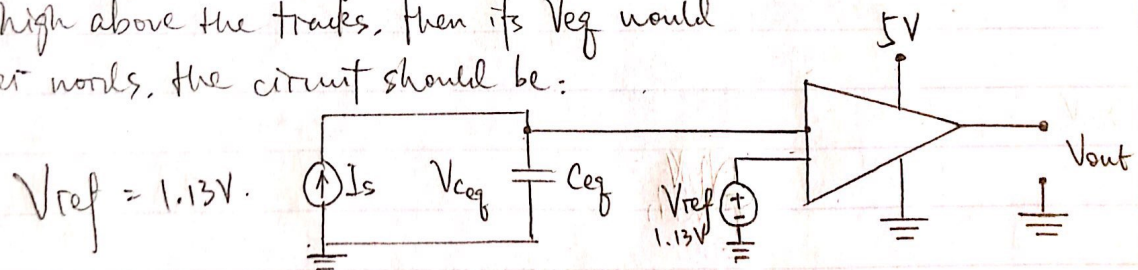which gives that the maximum V_{eq} for the train is 1.13 V ,
 and when it's too high above the tracks, then its V_{eq} would
 increase. In other words, the circuit should be:



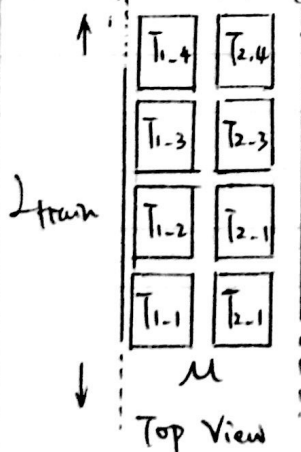- f). The design should be that the strips of metal, T_1 and T_2 , should be segmented into four pieces, and have sensors attached to each piece so that each op-amp comparator works independently to check the location they're measuring, respectively.
 i.e. The strip T_1 should be broken into one smaller strip per desired location, and similarly (symmetrically) for T_2 , which should look like:




Then, for any two strips T_{1-i} , T_{2-i} , $i \in [1, 4]$,

have an individual circuit hooked up to the two strips.

In this way, we could measure the height of the train at 4 different locations if the magnets (smaller strips) are placed at these 4 locations.

2. DRAM.

Given that $V_c(t) = \frac{I \cdot t}{C} + V_c(0)$, $V_c(0) = 1.2 \text{ V}$, $C = 18 \text{ fF}$

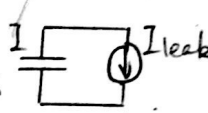and $I = I_{\text{leak}}$ as we could view the right half of the diagram as  which gives this relationship using KCL.

Thus, for $V_{\text{bit}} = V_c(t) > 0.8 \text{ V}$ and $t > 1 \text{ ms}$,

$$\text{So } I = \frac{(V_{\text{cell}} - V_c(0)) \cdot C}{t} < \frac{(1.2 \text{ V} - 0.8 \text{ V}) \cdot 18 \cdot 10^{-15} \text{ F}}{1 \cdot 10^{-3} \text{ s}} = 7.2 \text{ pA}$$

Thus, the maximum value of I_{leak} is $\boxed{7.2 \text{ pA}}$ ($7.2 \times 10^{-12} \text{ A}$).

3. (a). Since it's a current source and the capacitors are in series, using KCL,
so $I_{C_2} = I_s$, and so $\Rightarrow V_{out}(t) = \frac{I_{C_2} \cdot t}{C_2} + V_{C_2}(0) = \boxed{\frac{I_s \cdot t}{C_2}}$
and with $V_{C_2}(0) = 0V$.


b) Since $C_{eq2,3} = C_2 // C_3 = \frac{C_2 C_3}{C_2 + C_3}$, so $C_{eq} = C_1 + C_{eq2,3}$,

so first, $\frac{dV_s}{dt} = \frac{I_s}{C_{eq}}$ and so $I_s = C_{eq} \cdot \frac{dV_s}{dt}$


Using similar logic, so $I_{2,3} = C_{eq2,3} \cdot \frac{dV_s}{dt}$, which gives the proportionality

that $\frac{I_s}{C_{eq}} = \frac{I_{2,3}}{C_{eq2,3}}$, so $I_{2,3} = \frac{C_2 C_3}{C_1 C_2 + C_2 C_3 + C_3 C_1} \cdot I_s$


Thus, $V_{out}(t) = \frac{I_{2,3}}{C_3} \cdot t + \underset{\substack{\downarrow \\ 0V}}{V_{e_s}(0)} = \left| \frac{C_2}{C_1 C_2 + C_2 C_3 + C_3 C_1} \cdot I_s \cdot t \right|$

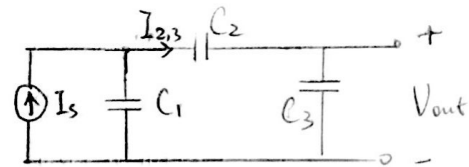


4. (a). Config 1.

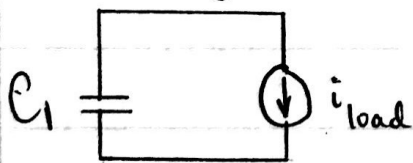

Config 2.

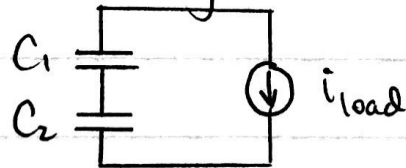

Config 3.

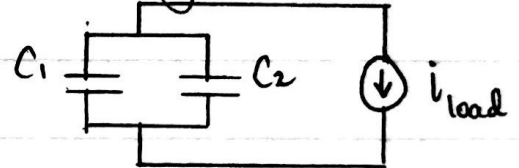

(b) ii) Config 1: $V_c(t) = \frac{I}{C} (t - t_0) + V_c(t_0)$. Using given information, so:

$$V(t) = V_c(t) = \frac{-i_{load}}{C_{sc}} (t - 0) + V_{init} = \boxed{-\frac{i_{load}}{C_{sc}} \cdot t + V_{init}}$$

→ ii) Config 2: Similarly, with the same basic equation and the fact that parallel capacitors gives: $V_c(t_0) = 2V_{init}$ and $C_{eq} = C_{sc} // C_{sc} = \frac{C_{sc}}{2}$

$$\text{So, } V(t) = V_c(t) = \frac{-i_{load}}{\frac{1}{2} C_{sc}} (t - 0) + 2 \cdot V_{init} = \boxed{-\frac{2i_{load}}{C_{sc}} \cdot t + 2V_{init}}$$

→ iii) Config 3: Again, $V_c(t_0) = V_{sc}(t_0) = V_{init}$ and $C_{eq} = C_{sc} + C_{sc} = 2C_{sc}$ (in series)

$$\text{Thus, } V(t) = V_c(t) = \frac{-i_{load}}{2C_{sc}} (t - 0) + V_{init} = \boxed{-\frac{i_{load}}{2C_{sc}} \cdot t + V_{init}}$$

(c) (i) Config 1. For the device to function properly, so $V(t) \geq V_{min}$, so we have

$$-\frac{i_{load}}{C_{sc}} \cdot t + V_{init} \geq V_{min} \Rightarrow \frac{i_{load}}{C_{sc}} \cdot t \leq V_{init} - V_{min}$$

so, $t \leq (V_{init} - V_{min}) \cdot \frac{C_{sc}}{i_{load}}$, which is the life time is:

$$t_{life1} = \left\lfloor (V_{init} - V_{min}) \cdot \frac{C_{sc}}{i_{load}} \right\rfloor$$

→ (ii) Config 2. Similarly, so: $-\frac{2i_{load}}{C_{sc}} \cdot t + 2V_{init} \geq V_{min}$
 $\Rightarrow t \leq (2V_{init} - V_{min}) \cdot \frac{C_{sc}}{2i_{load}}$

which gives that $t_{life2} = \left\lfloor (2V_{init} - \frac{1}{2}V_{min}) \cdot \frac{C_{sc}}{i_{load}} \right\rfloor$

→ (iii) Config 3. Again, similarly we have $-\frac{i_{load}}{2C_{sc}} \cdot t + V_{init} \geq V_{min}$
 $\Rightarrow t \leq (V_{init} - V_{min}) \cdot \frac{2C_{sc}}{i_{load}}$

Thus, $t_{life3} = \left\lfloor (2V_{init} - 2V_{min}) \cdot \frac{C_{sc}}{i_{load}} \right\rfloor$

(d) To have Config 3 better than Config 2, so $t_{life3} > t_{life2}$,

which is equivalent to: $(2V_{init} - 2V_{min}) \cdot \frac{C_{sc}}{i_{load}} > (V_{init} - \frac{1}{2}V_{min}) \cdot \frac{C_{sc}}{i_{load}}$

$$\Rightarrow 2V_{init} - 2V_{min} > V_{init} - \frac{1}{2}V_{min}$$

$$\Rightarrow V_{init} > \frac{3}{2}V_{min}$$

Thus, under the condition that $V_{init} > \frac{3}{2}V_{min}$ only is Config 3 better than 2.

5. (a) When tank is full, the entire capacitor has permittivity of water, 81ϵ .
 so, $C_{eq} = C_{H_2O} = 81\epsilon \cdot \frac{h_{tot} \cdot w}{d} = \boxed{81\epsilon \cdot h_{tot}}$
 When it's empty, the entire capacitor is air, with permittivity ϵ .
 so, $C_{eq} = C_{air} = \epsilon \cdot \frac{h_{total} \cdot w}{d} = \boxed{\epsilon \cdot h_{tot}}$

(b) Here, two capacitors act in parallel, and we have $C_{tank} = C_{H_2O} \parallel C_{air}$,
 with $C_{H_2O} = 81\epsilon \cdot \frac{h_{H_2O} \cdot w}{d} = 81\epsilon \cdot h_{H_2O}$
 and $C_{air} = \epsilon \cdot \frac{(h_{tot} - h_{H_2O}) \cdot w}{d} = \epsilon \cdot (h_{tot} - h_{H_2O})$

$$\text{Thus, } C_{tank} = \frac{C_{H_2O} \cdot C_{air}}{C_{H_2O} + C_{air}} = \frac{81\epsilon^2 h_{H_2O} (h_{tot} - h_{H_2O})}{80\epsilon h_{H_2O} + \epsilon \cdot h_{tot}} = \boxed{\frac{81\epsilon h_{H_2O} (h_{tot} - h_{H_2O})}{80 h_{H_2O} + h_{tot}}}$$

(c) $V_c(t) = \frac{I_s}{C_{tank}} \cdot t + V_c(0)$ and since $V_c(0) = 0V$, so $V_c(t) = \boxed{\frac{I_s}{C_{tank}} \cdot t}$

(d) By measuring V_c for a brief amount of time, we could easily (and successfully) determine t in seconds and $V_c(t)$ in V. Since I_s is a known current source, so $C_{tank} = \frac{I_s}{V_c(t)} \cdot t$ could be calculated. ✓

Then, using the capacitance of C_{tank} calculated, with ϵ, h_{tot} being known, so we can determine h_{H_2O} with this equation, so h_{H_2O} can be determined as well in this way. ✓

6. (a) Using a voltage divider, so $V_+ = \frac{R_{fixed}}{R_{photo} + R_{fixed}} \cdot 5V$.

(b) Using the given info, so we want $3V = \frac{R_{fixed}}{1k\Omega + R_{fixed}} \cdot 5V \Rightarrow R_{fixed} = 1.5k\Omega$.

(c) Since we can divide the situation into two cases, exactly one of them must be true:
 (1) $V_+ > V_- = 2.5V$ or (2) $V_+ < V_- = 2.5V$, so:

Case (1): $V_+ > 2.5V$, since the op-amp is ideal, so

$$V_{out} = 5V \text{ when } V_+ > 2.5V$$

Case (2): $V_+ < 2.5V$, again similarly, so

$$V_{out} = 0V \text{ when } V_+ < 2.5V$$

(d) The condition $V_+ > 2.5V$ is equivalent to $\frac{1.5k\Omega}{R_{photo} + 1.5k\Omega} \cdot 5V > 2.5V \Rightarrow R_{photo} < 1.5k\Omega$

Similarly, $V_+ < 2.5V$ is equivalent to $R_{photo} > 1.5k\Omega$.

Thus,

$$V_{out} = \begin{cases} 5V & \text{when } R_{photo} < 1.5k\Omega \\ 0V & \text{when } R_{photo} > 1.5k\Omega \end{cases}$$

(e) When we want $I_{LED} = 20mA$ when the photoresistor is in the "light" condition,

so $V_{out} = 5V$, and we have that $R_{lim} = \frac{V_{lim}}{I_{lim}} = \frac{V_{out} - V_{LED}}{I_{LED}} = \frac{5V - 3V}{20mA} = 100\Omega$.

7. Homework Process and Study Group

I worked alone without getting any help, except asking questions and reading posts (especially answers from the GSIs) on Piazza as well as reading the Notes of the course.