

Since we can verify that the op-amp is in negative feedback, so the Golden Rules gives:

$$i_1 = i_2 = 0$$

$$V_+ = V_- = 0 \text{ (grounded } V_+)$$

Then, using KCL, so  $i_1 = i_2 + i_c \Rightarrow i_1 = i_c$

Then, since  $V_o - V_+ = V_{R_1} = i_1 \cdot R_1$  with  $V_+ = 0$ .

$$\text{so } i_c = i_1 = \frac{V_o}{R_1}$$

$$\text{Now, } V_1 - V_+ = -V_{C_1} \Rightarrow V_1 = -V_{C_1} \quad (1)$$

which could be calculated by having  $i_c = C_1 \frac{dV_{C_1}}{dt} = \frac{V_o}{R_1}$

$$\Rightarrow \int_0^t dV_{C_1} = \int_0^t \frac{V_o}{R_1 C_1} dt$$


$$\Rightarrow V_{C_1}(t) - V_{C_1}(0) = \frac{V_o}{R_1 C_1} (t - 0)$$

with  $V_{C_1}(0) = 0V$ , so  $V_{C_1}(t) = \frac{V_o}{R_1 C_1} t$


$$\Rightarrow V_1 = -V_{C_1} = \boxed{-\frac{V_o \cdot t}{R_1 C_1}}$$

$$b) T_1 = T_2 = \frac{-V_{TH} - V_{TN}}{-\frac{V_{SAT}}{R_1 C_1}} = \frac{2V_{TH} R_1 C_1}{V_{SAT}}$$

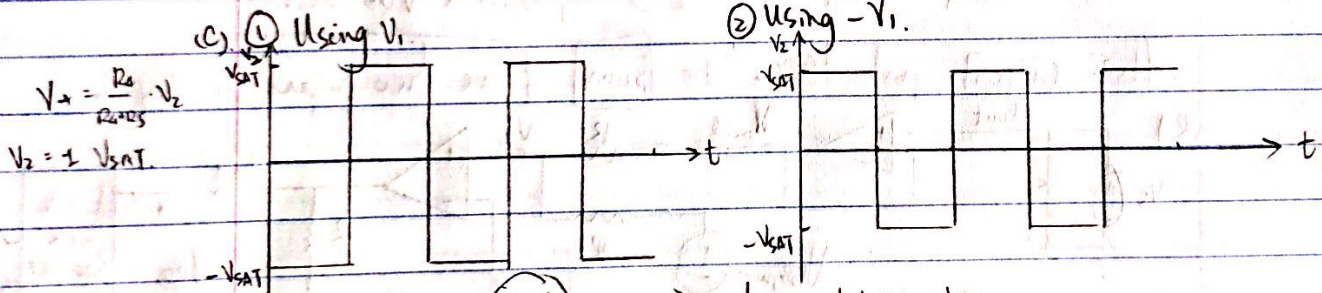by analyzing the eq 1 line and its slope given.



With  $-V_1$  as input matches (b)

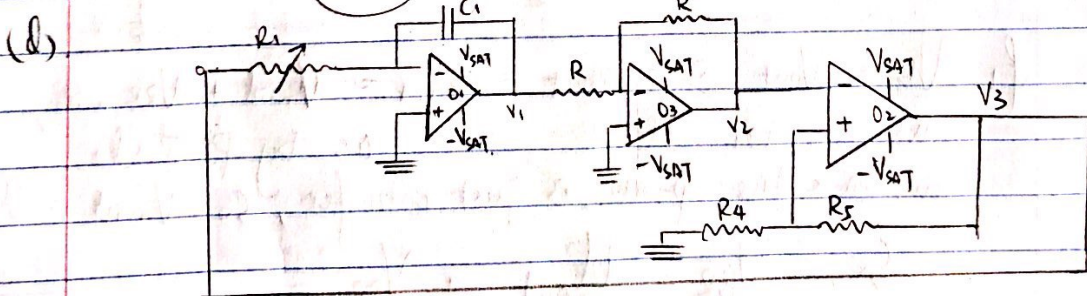

(e) First,  $+V_{TH} = \frac{R_4}{R_4 + R_5} V_{SAT}$ . with  $+V_{SAT} = 10V$ ,  $C_1 = 0.01mF$ ,  $R_4 = 10k\Omega$ , and  $+V_{TH} = 5V$ , so  $R_5 = 10k\Omega$ .

Then, since we wish to have  $f = 1kHz$ , so  $t = \frac{1}{f} = 1ms$ .

So  $R_1 C_1 = 1ms$ , with  $C_1 = 0.01mF$ ,

so  $R_1 = 100\Omega$


$$\Rightarrow \boxed{R_1 = 100\Omega, R_5 = 10k\Omega}$$



2. (a)  $\bigcirc I_s$   $\bigcirc V_s$   $\bullet R_1$   $\bigcirc R_2$   $\bigcirc R_3$   $\bigcirc R_4$   
 (MT Q3) (b)  $\bullet U_1$   $\bullet U_2$   $\bullet U_3$   $\bigcirc U_4$   $\bigcirc U_5$   $\bigcirc U_6$   
 (c)  $U_5 - U_4 = i_3 R_3$   
 (d)  $i_3 + i_2 - i_4 = 0$

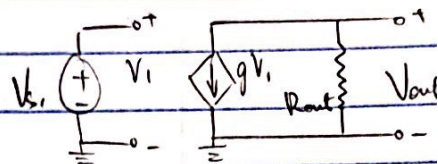3. (a) Due to the direction of the current,  
 (MT Q4) we have that  $V_{out,1} = -gV_1 R_{out}$ .

Then,  $V_1 = V_{s1}$ , so  $V_{out,1} = -gV_{s1} R_{out}$



(b) Similarly,  $V_{out,2} = -gV_2 R_{out} = -gV_{s2} R_{out}$

(c) Thus,  $V_{out} = V_{out,1} + V_{out,2} = -gV_{s1} R_{out} - gV_{s2} R_{out}$

With  $g = \frac{1}{R_{out}}$ , so  $V_{out} = -V_{s1} - V_{s2}$

(d) Now,  $V_{Th} = V_{out} = -V_{s1} - V_{s2}$  as calculated in part (c).


Then, we can zero all the independent sources and calculate  $I_{test}$

So  $V_1 = V_2 = V_{s1} = V_{s2} = 0V$ , so  $gV_1 = gV_2 = 0(A)$ .

Supplying a  $V_{test}$ , we have  $I_{test} = \frac{V_{test}}{R_{out}}$

So  $R_{Th} = \frac{V_{test}}{I_{test}} = R_{out}$

Thus, the Thevenin equivalent is:

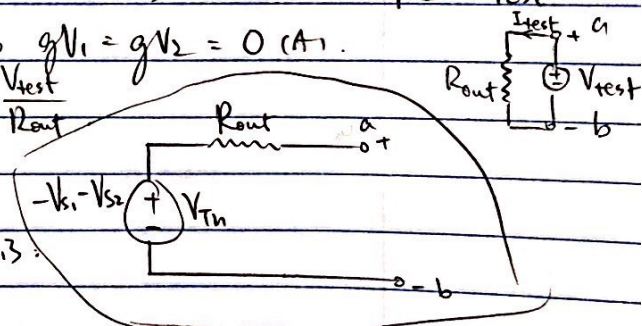

4. (a) Using voltage divider,  $V_{Daisy} = \frac{4k\Omega}{4k\Omega + 4k\Omega} \cdot 1kV = 500V$ .

(MT Q5).

So  $W_{Daisy} = \frac{V_{Daisy}^2}{R_{Daisy}} = \frac{(500V)^2}{4k\Omega} = 62.5W > 10W = W_{breakdown}$ .

So, Daisy is not safe.



(b)  $R_{eq} = R_{free} \parallel R_{Daisy} \parallel R_{Btlon} = 4k\Omega \parallel 4k\Omega \parallel 2k\Omega = 1k\Omega$   
 $\Rightarrow V_{Daisy} = V_{Btlon} = \frac{1k\Omega}{4k\Omega + 1k\Omega} \cdot 1kV = 200V$  using voltage divider.

$\Rightarrow W_{Daisy} = \frac{V_{Daisy}^2}{R_{Daisy}} = \frac{(200V)^2}{4k\Omega} = 10W \leq W_{Daisy, breakdown}$

$W_{Btlon} = \frac{V_{Btlon}^2}{R_{Btlon}} = \frac{(200V)^2}{2k\Omega} = 20W \leq 25W = W_{Btlon, breakdown}$

Thus, Both Daisy and Btlon are safe.

5. (12T Q6)

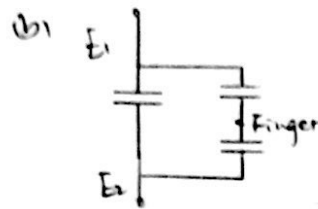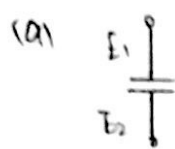

(c)  $C = \epsilon \frac{A}{d}$   
 $= (12 \text{ fF/mm} + n \text{ fF/mm}) \cdot \frac{A}{d}$   
 $= \left[ (12+n) \cdot \frac{A}{d} \text{ fF/mm} \right]$

(1) i. This is when the finger is touching,

So  $C_{\text{touch}} = C_{\text{no touch}} + (C_{F-E1} \parallel (C_{F-E1L} + C_{F-E2R}))$   
 $= (12+n) \cdot \frac{4 \text{ mm}^2}{2 \text{ mm}} \text{ fF/mm} + 8 \text{ fF} \parallel (4 \text{ fF} + 4 \text{ fF})$   
 $= (24 + 2n) \text{ fF} + 4 \text{ fF} = \boxed{(28 + 2n) \text{ fF}}$

(2) No touch is when the other branch is open circuit,

So  $C_{\text{no touch, eq}} = C_{\text{no touch}} = \boxed{(24 + 2n) \text{ fF}}$

Thus, we can calculate.  $\frac{(28+2n) \text{ fF} - (24+2n) \text{ fF}}{(24+2n) \text{ fF}} \geq 10\%$   
 for the display to work:

$\Rightarrow 4 \geq 2.4 + 0.2n$

So  $n \leq 8$

Thus, maximum fire times is  $\boxed{8}$

6(a), Since  $I_c = -I_{PD}$  and  $I_c = C_{PD} \frac{dV_{PD}}{dt}$   
 (12T Q7)


So  $-I_{PD} = C_{PD} \frac{dV_{PD}}{dt}$

$\Rightarrow \int_0^t \frac{-I_{PD}}{C_{PD}} dt = \int_0^t dV_{PD}$


$\Rightarrow -\frac{I_{PD}}{C_{PD}} (t-t_0) = V_{PD}(t) - V_{PD}(0)$

and given that  $V_{PD}(t_{z0}) = V_{DD}$ ,

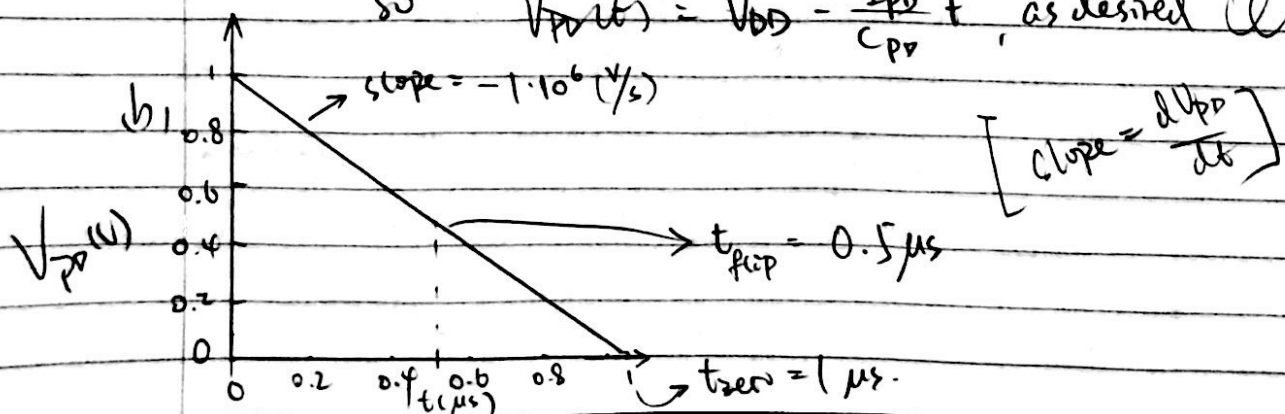So  $V_{PD}(t) = V_{DD} - \frac{I_{PD}}{C_{PD}} t$ , as desired (Q.E.D.)





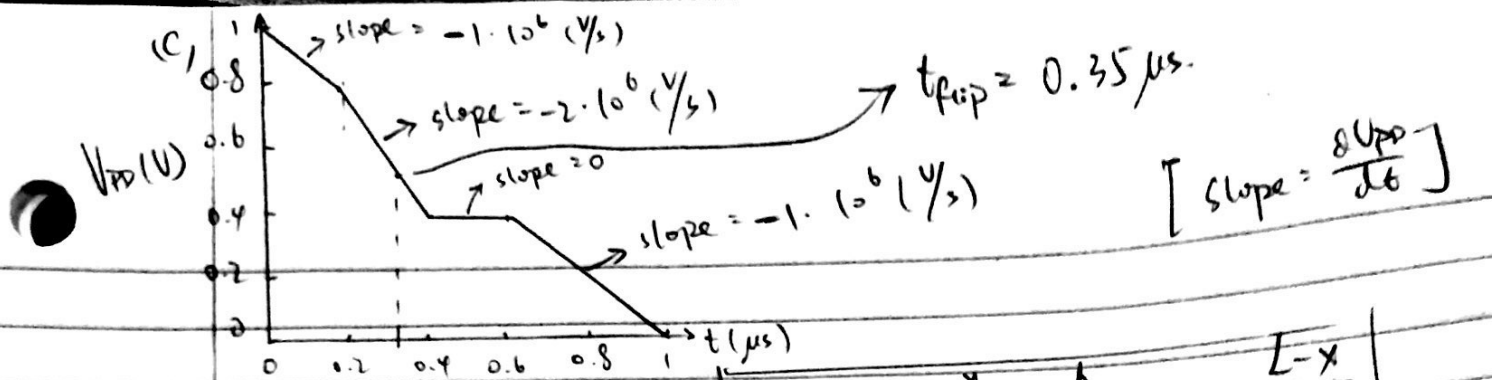


7. (MT a8) (a) Since  $R = \rho \frac{L}{A}$ , so  $R_{\text{bottom}} = \rho \frac{x}{A}$ ,  $R_{\text{top}} = \rho \frac{L-x}{A}$

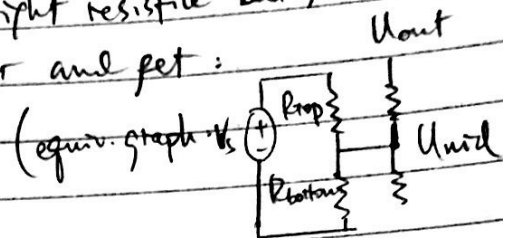(b) Since there's no current through the right resistive bar,

so we can use just a voltage divider and get:

$$U_{\text{mid}} = U_{\text{out}} = \frac{R_{\text{bottom}}}{R_{\text{top}} + R_{\text{bottom}}} V_s$$



(c) No because  $U_{\text{out}}$  can go as low as 0V


with  $x \rightarrow 0$ . But  $V_{BB, \text{min}} > 0$ , so we can't utilize the full range.

(d) First  $V_+ = \frac{R}{2+R} V_{\text{in}} + \frac{R}{2+R} V_{BB, \text{min}}$   
 $= \frac{1}{2} (V_{\text{in}} + V_{BB, \text{min}})$

Then, using formula for a non-inverting negative feedback op-amp,

$$\text{so } V_{\text{out}} = V_+ \cdot \left(1 + \frac{R}{R}\right) = V_{\text{in}} + V_{BB, \text{min}}$$

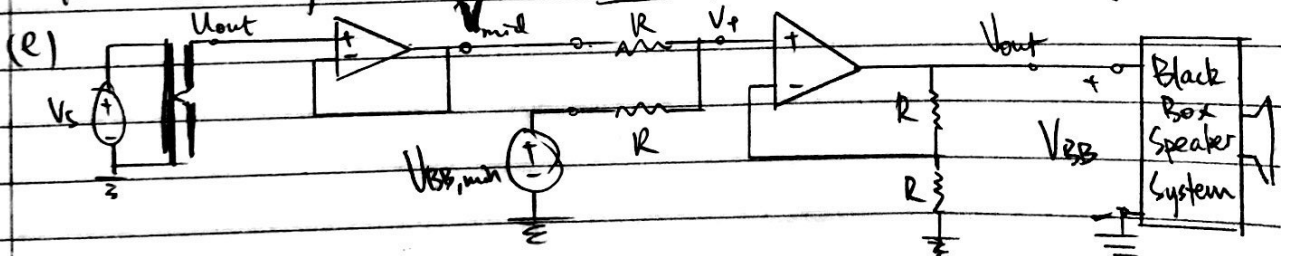This circuit just takes the Sum of the two input voltages.



f)  $V_{BB} = V_{\text{out}} - 0 = V_{\text{out}} = 2V_+ = U_{\text{mid}} + V_{BB, \text{min}}$   
 as by part (d).

Then, since the op-amp is just a buffer, so  $U_{\text{mid}} = U_{\text{out}}$

So,  $V_{BB} = U_{\text{out}} + V_{BB, \text{min}}$

$$= \frac{R_{\text{bottom}}}{R_{\text{top}} + R_{\text{bottom}}} V_s + V_{BB, \text{min}} = \left[ \frac{x}{L} V_s + V_{BB, \text{min}} \right]$$

g) I'd like "like"

⇒ 8. I worked alone without help, except memory from MT and Discussion.