


1. Maglev.

(b)  They're connected to each other in series.

(c)  $C_{eq} = C_{T1} \parallel C_{T2} = \frac{C_{T1} C_{T2}}{C_{T1} + C_{T2}} = \frac{C_{T1}^2}{2 C_{T1}}$  with  $C_{T1} = C_{T2} \neq 0$ , so cancelling.

Thus,  $C_{eq} = \frac{C_{T1}}{2} = \left[ 4.425 \cdot 10^{-12} \text{ F/m} \cdot \frac{L_{\text{train}} \cdot W}{h} \right]$

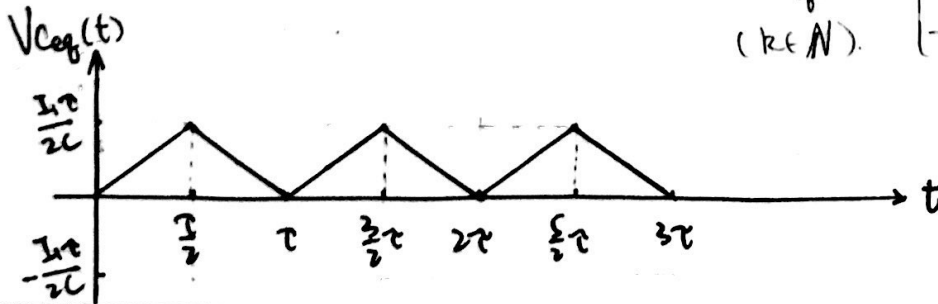
(d) Since at  $t=0$ ,  $V_{eq}(0) = 0V$ , and when a constant current source is applied, we have  $V_{eq}(t) = \frac{1}{C} t + V_{eq}(0)$ , and since  $I_s$  is constant from  $t=0$  to  $t = \frac{\tau}{2}$ , so  $V_{eq}(t) = \frac{1}{C} t$  for  $t \in [0, \frac{\tau}{2}]$ . Using similar logic as Note 17, we have  $V_{eq}(t) = \frac{1}{C} (t - t_0) + V_{eq}(t_0)$  and so here we supply each period ( $\frac{\tau}{2}$ ) of constant current, so the voltage pattern mimics the one on the note 17, and thus is:  $V_{eq}(t) = \begin{cases} \frac{I_s}{C_{eq}} (t - k\tau) & \text{when } k\tau \leq t \leq (k + \frac{1}{2})\tau \\ -\frac{I_s}{C_{eq}} (t - k\tau - \frac{\tau}{2}) + \frac{I_s \tau}{2C_{eq}} & \text{when } (k + \frac{1}{2})\tau \leq t \leq (k+1)\tau \end{cases}$  ( $k \in \mathbb{N}$ ).




(c). When  $d < 1\text{ cm}$  then  $C_{eq} = 4.425 \cdot 10^{-12} \text{ F/m} \cdot \frac{L_{train} \cdot w}{d} > 4.425 \cdot 10^{-12} \text{ F/m} \cdot \frac{100\text{m} \cdot 1\text{cm}}{1\text{cm}}$   
 with  $L_{train} = 100\text{m}$ ,  $w = 1\text{cm}$ , so,  $C_{eq} > 4.425 \cdot 10^{-10} \text{ F}$ .

$$\text{Thus, } V_{Ceq} \leq \frac{I_s \cdot t}{2C_{eq}} < \frac{1\text{mA} \cdot 1\mu\text{s}}{2 \cdot 4.425 \cdot 10^{-10} \text{ F}} = 1.13 \text{ V}$$

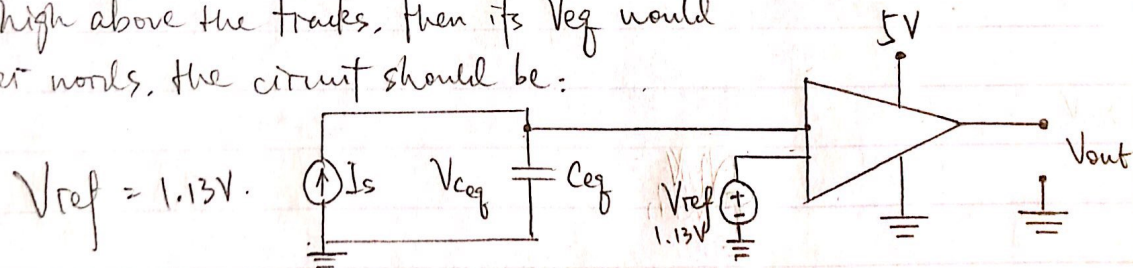which gives that the maximum  $V_{eq}$  for the train is  $1.13 \text{ V}$ ,  
 and when it's too high above the tracks, then its  $V_{eq}$  would  
 increase. In other words, the circuit should be:



- f). The design should be that the strips of metal,  $T_1$  and  $T_2$ , should be segmented into four pieces, and have sensors attached to each piece so that each op-amp comparator works independently to check the location they're measuring, respectively.  
 i.e. The strip  $T_1$  should be broken into one smaller strip per desired location, and similarly (symmetrically) for  $T_2$ , which should look like:

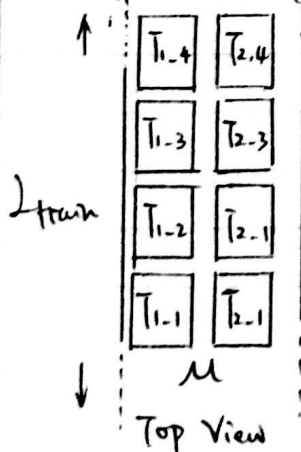


Then, for any two strips  $T_{1-i}$ ,  $T_{2-i}$ ,  $i \in [1, 4]$ ,

have an individual circuit hooked up to the two strips.

In this way, we could measure the height of the train at 4 different locations if the magnets (smaller strips) are placed at these 4 locations.

2. DRAM.

Given that  $V_c(t) = \frac{I \cdot t}{C} + V_c(0)$ ,  $V_c(0) = 1.2 \text{ V}$ ,  $C = 18 \text{ fF}$

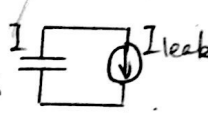and  $I = I_{\text{leak}}$  as we could view the right half of the diagram as  which gives this relationship using KCL.

Thus, for  $V_{\text{bit}} = V_c(t) > 0.8 \text{ V}$  and  $t > 1 \text{ ms}$ ,

$$\text{So } I = \frac{(V_{\text{cell}} - V_c(0)) \cdot C}{t} < \frac{(1.2 \text{ V} - 0.8 \text{ V}) \cdot 18 \cdot 10^{-15} \text{ F}}{1 \cdot 10^{-3} \text{ s}} = 7.2 \text{ pA}$$

Thus, the maximum value of  $I_{\text{leak}}$  is  $\boxed{7.2 \text{ pA}}$  ( $7.2 \times 10^{-12} \text{ A}$ ).

3. (a). Since it's a current source and the capacitors are in series, using KCL,  
so  $I_{C_2} = I_s$ , and so  $\Rightarrow V_{out}(t) = \frac{I_{C_2} \cdot t}{C_2} + V_{C_2}(0) = \boxed{\frac{I_s \cdot t}{C_2}}$   
and with  $V_{C_2}(0) = 0V$ .


b) Since  $C_{eq2,3} = C_2 // C_3 = \frac{C_2 C_3}{C_2 + C_3}$ , so  $C_{eq} = C_1 + C_{eq2,3}$ ,

so first,  $\frac{dV_s}{dt} = \frac{I_s}{C_{eq}}$  and so  $I_s = C_{eq} \cdot \frac{dV_s}{dt}$


Using similar logic, so  $I_{2,3} = C_{eq2,3} \cdot \frac{dV_s}{dt}$ , which gives the proportionality

that  $\frac{I_s}{C_{eq}} = \frac{I_{2,3}}{C_{eq2,3}}$ , so  $I_{2,3} = \frac{C_2 C_3}{C_1 C_2 + C_2 C_3 + C_3 C_1} \cdot I_s$


Thus,  $V_{out}(t) = \frac{I_{2,3}}{C_3} \cdot t + \underset{\substack{\downarrow \\ 0V}}{V_{e_s}(0)} = \left| \frac{C_2}{C_1 C_2 + C_2 C_3 + C_3 C_1} \cdot I_s \cdot t \right|$

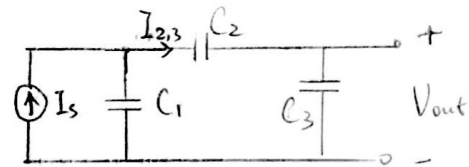


4. (a). Config 1.

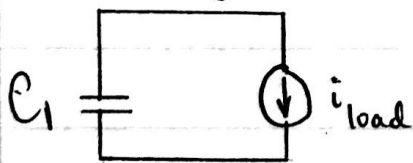

Config 2.

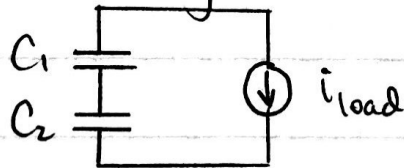

Config 3.

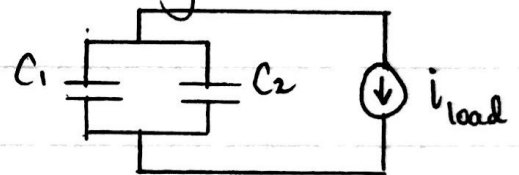

(b) ii) Config 1:  $V_c(t) = \frac{I}{C} (t - t_0) + V_c(t_0)$ . Using given information, so:

$$V(t) = V_c(t) = \frac{-i_{load}}{C_{sc}} (t - 0) + V_{init} = \boxed{-\frac{i_{load}}{C_{sc}} \cdot t + V_{init}}$$

→ ii) Config 2: Similarly, with the same basic equation and the fact that parallel capacitors gives:  $V_c(t_0) = 2V_{init}$  and  $C_{eq} = C_{sc} // C_{sc} = \frac{C_{sc}}{2}$

$$\text{So, } V(t) = V_c(t) = \frac{-i_{load}}{\frac{1}{2} C_{sc}} (t - 0) + 2 \cdot V_{init} = \boxed{-\frac{2i_{load}}{C_{sc}} \cdot t + 2V_{init}}$$

→ iii) Config 3: Again,  $V_c(t_0) = V_{sc}(t_0) = V_{init}$  and  $C_{eq} = C_{sc} + C_{sc} = 2C_{sc}$  (in series)

$$\text{Thus, } V(t) = V_c(t) = \frac{-i_{load}}{2C_{sc}} (t - 0) + V_{init} = \boxed{-\frac{i_{load}}{2C_{sc}} \cdot t + V_{init}}$$



(c) (i) Config 1. For the device to function properly, so  $V(t) \geq V_{min}$ , so we have

$$-\frac{i_{load}}{C_{sc}} \cdot t + V_{init} \geq V_{min} \Rightarrow \frac{i_{load}}{C_{sc}} \cdot t \leq V_{init} - V_{min}$$

so,  $t \leq (V_{init} - V_{min}) \cdot \frac{C_{sc}}{i_{load}}$ , which is the life time is:

$$t_{life1} = \left\lfloor (V_{init} - V_{min}) \cdot \frac{C_{sc}}{i_{load}} \right\rfloor$$

→ (ii) Config 2. Similarly, so:  $-\frac{2i_{load}}{C_{sc}} \cdot t + 2V_{init} \geq V_{min}$   
 $\Rightarrow t \leq (2V_{init} - V_{min}) \cdot \frac{C_{sc}}{2i_{load}}$

which gives that  $t_{life2} = \left\lfloor (2V_{init} - \frac{1}{2}V_{min}) \cdot \frac{C_{sc}}{i_{load}} \right\rfloor$

→ (iii) Config 3. Again, similarly we have  $-\frac{i_{load}}{2C_{sc}} \cdot t + V_{init} \geq V_{min}$   
 $\Rightarrow t \leq (V_{init} - V_{min}) \cdot \frac{2C_{sc}}{i_{load}}$

Thus,  $t_{life3} = \left\lfloor (2V_{init} - 2V_{min}) \cdot \frac{C_{sc}}{i_{load}} \right\rfloor$

(d) To have Config 3 better than Config 2, so  $t_{life3} > t_{life2}$ ,

which is equivalent to:  $(2V_{init} - 2V_{min}) \cdot \frac{C_{sc}}{i_{load}} > (V_{init} - \frac{1}{2}V_{min}) \cdot \frac{C_{sc}}{i_{load}}$

$$\Rightarrow 2V_{init} - 2V_{min} > V_{init} - \frac{1}{2}V_{min}$$

$$\Rightarrow V_{init} > \frac{3}{2}V_{min}$$

Thus, under the condition that  $V_{init} > \frac{3}{2}V_{min}$  only is Config 3 better than 2.

5. (a) When tank is full, the entire capacitor has permittivity of water,  $81\epsilon$ .  
 so,  $C_{eq} = C_{H_2O} = 81\epsilon \cdot \frac{h_{tot} \cdot w}{d} = \boxed{81\epsilon \cdot h_{tot}}$   
 When it's empty, the entire capacitor is air, with permittivity  $\epsilon$ .  
 so,  $C_{eq} = C_{air} = \epsilon \cdot \frac{h_{total} \cdot w}{d} = \boxed{\epsilon \cdot h_{tot}}$

- (b) Here, two capacitors act in parallel, and we have  $C_{tank} = C_{H_2O} \parallel C_{air}$ ,  
 with  $C_{H_2O} = 81\epsilon \cdot \frac{h_{H_2O} \cdot w}{d} = 81\epsilon \cdot h_{H_2O}$   
 and  $C_{air} = \epsilon \cdot \frac{(h_{tot} - h_{H_2O}) \cdot w}{d} = \epsilon \cdot (h_{tot} - h_{H_2O})$

$$\text{Thus, } C_{tank} = \frac{C_{H_2O} \cdot C_{air}}{C_{H_2O} + C_{air}} = \frac{81\epsilon^2 h_{H_2O} (h_{tot} - h_{H_2O})}{80\epsilon h_{H_2O} + \epsilon \cdot h_{tot}} = \boxed{\frac{81\epsilon h_{H_2O} (h_{tot} - h_{H_2O})}{80 h_{H_2O} + h_{tot}}}$$

- (c)  $V_c(t) = \frac{I_s}{C_{tank}} \cdot t + V_c(0)$  and since  $V_c(0) = 0V$ , so  $V_c(t) = \boxed{\frac{I_s}{C_{tank}} \cdot t}$

- (d) By measuring  $V_c$  for a brief amount of time, we could easily (and successfully) determine  $t$  in seconds and  $V_c(t)$  in V. Since  $I_s$  is a known current source, so  $C_{tank} = \frac{I_s}{V_c(t)} \cdot t$  could be calculated. ✓

Then, using the capacitance of  $C_{tank}$  calculated, with  $\epsilon, h_{tot}$  being known, so we can determine  $h_{H_2O}$  with this equation, so  $h_{H_2O}$  can be determined as well in this way. ✓

6. (a) Using a voltage divider, so  $V_+ = \frac{R_{fixed}}{R_{photo} + R_{fixed}} \cdot 5V$ .

(b) Using the given info, so we want  $3V = \frac{R_{fixed}}{1k\Omega + R_{fixed}} \cdot 5V \Rightarrow R_{fixed} = 1.5k\Omega$ .

(c) Since we can divide the situation into two cases, exactly one of them must be true:  
 (1)  $V_+ > V_- = 2.5V$  or (2)  $V_+ < V_- = 2.5V$ , so:

Case (1):  $V_+ > 2.5V$ , since the op-amp is ideal, so

$$V_{out} = 5V \text{ when } V_+ > 2.5V$$

Case (2):  $V_+ < 2.5V$ , again similarly, so

$$V_{out} = 0V \text{ when } V_+ < 2.5V$$

(d) The condition  $V_+ > 2.5V$  is equivalent to  $\frac{1.5k\Omega}{R_{photo} + 1.5k\Omega} \cdot 5V > 2.5V \Rightarrow R_{photo} < 1.5k\Omega$

Similarly,  $V_+ < 2.5V$  is equivalent to  $R_{photo} > 1.5k\Omega$ .

Thus,

$$V_{out} = \begin{cases} 5V & \text{when } R_{photo} < 1.5k\Omega \\ 0V & \text{when } R_{photo} > 1.5k\Omega \end{cases}$$

(e) When we want  $I_{LED} = 20mA$  when the photoresistor is in the "light" condition,

so  $V_{out} = 5V$ , and we have that  $R_{lim} = \frac{V_{lim}}{I_{lim}} = \frac{V_{out} - V_{LED}}{I_{LED}} = \frac{5V - 3V}{20mA} = 100\Omega$ .